

Lecture 2: Introduction to RISC-V, Register File, ALU

Xuan-Truong Nguyen



Recap: Course overview

#	Topics	Labs
1	Introduction, Basic Digital Logic	ModelSim, Encoder, Counter
2	Introduction to RISC-V	Register File, Shifter and ALU
3	Instruction Set Architecture	Instruction memory, decoder
4	Instructions	Program Counter, Branch Instruction
5	RISC-V Compiler, GNU Tool Chain	Load/Store Instruction, RISC-V core
6	AMBA Bus Specification	AHB Master, AHB slave, AHB Bus
7	IO Devices and Display Panel	LCD Drive, Display Panel
8	System integration	LCD interface, memory interface, top system
9	Accelerator, Super resolution networks	Matlab, CNN reference S/W, quantization, BRAM
10	Computing Units of DNN accelerator	MAC, Adder tree, quantization, and activation
11	Datapath for a DNN accelerator I	Sliding windows, weight/bias/scale buffers
12	Datapath for a DNN accelerator II	Buffer access, Super resolution NPU
13	System Integration	BRAM, Function verification, DMA
14	Optimization	Dual buffering, Pipelining
15	Final project and Final Exam	Execution time reduction, Memory buffer reduction

Recap: Challenges with DNN Computations

- Millions of Parameters (i.e., weights)


- Billions of computations ➔ Need lots of parallel computations

DNN Topology	Number of Weights
AlexNet (2012)	3.98M
VGGnet-16 (2014)	28.25M
GoogleNet (2015)	6.77M
Resnet-50 (2016)	23M
DLRM (2019)	540M
Megatron (2019)	8.3B

This makes CPUs inefficient

- Heavy data movement

➔ Need to reduce energy

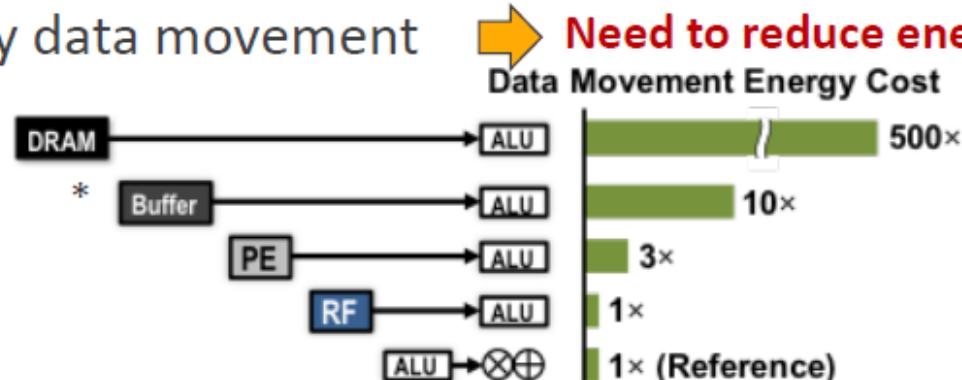


This makes GPUs inefficient

Ca

AI computing system

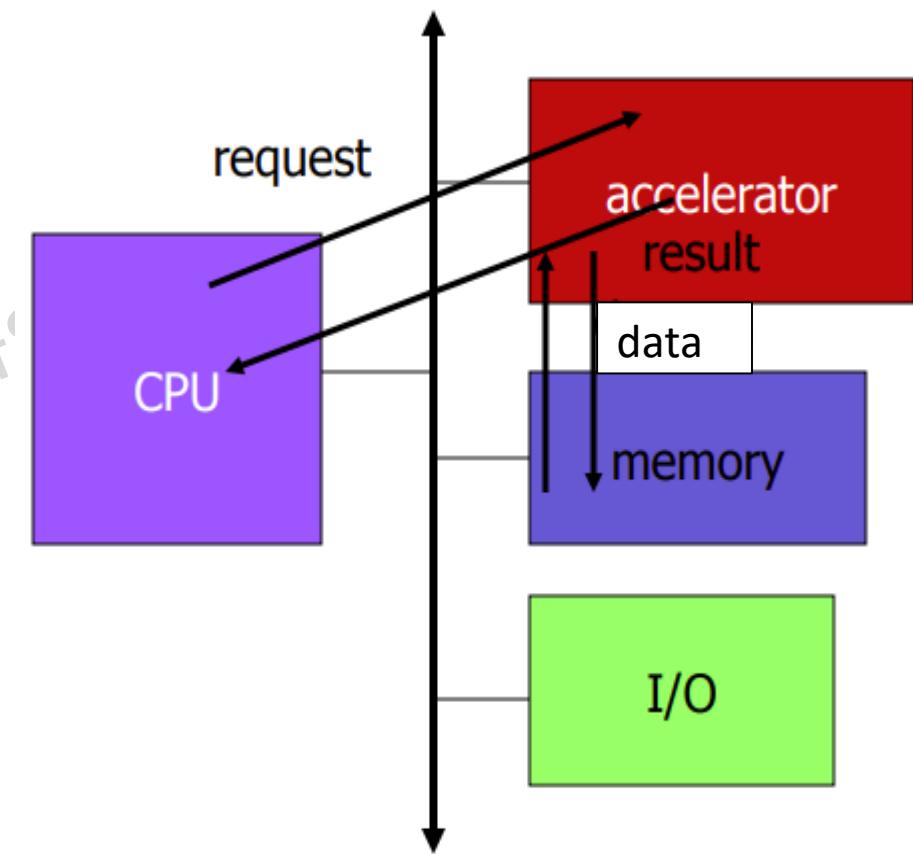- Von Neumann architecture
 - A central processing unit (CPU)
 - Memory
 - Input/Output (IO)
- AI or Deep Learning Accelerator
 - Use additional computational units dedicated to some functionality
 - A hardware (H/W) module for specified applications
- Hardware/software co-design
 - Joint design of H/W and S/W architectures



Lecture plan

- Today we will:
 - Study RISC-V
 - Continue reviewing Verilog HDL
 - Describe how to use continuous assignments
 - Describe the data types allowed in Verilog HDL
 - Describe the operation of the operators used in Verilog HDL
 - Describe the operands that may be used associated with a specified operator
(Credit: Some slides are based on Digital Systems Design and Experiments
(<https://ocw.snu.ac.kr/node/2390>))
- Labs
 - Lab 1: Register file
 - Lab 2: Shifter, Arithmetic unit
 - Lab 3: Multiplier

Road map

Computing
on RISC
operations.
Open source
architecture
based

Introduction to RISC-V


Verilog HDL
Dataflow modelling

Labs

The Computer Revolution

- Progress in computer technology
 - Underpinned by Moore's Law
- Makes novel applications feasible
 - Computers in automobiles
 - Cell phones
 - Human genome project
 - World Wide Web
 - Search Engines
- Computers are pervasive in our life.

THE TIMELINE OF COMPUTER

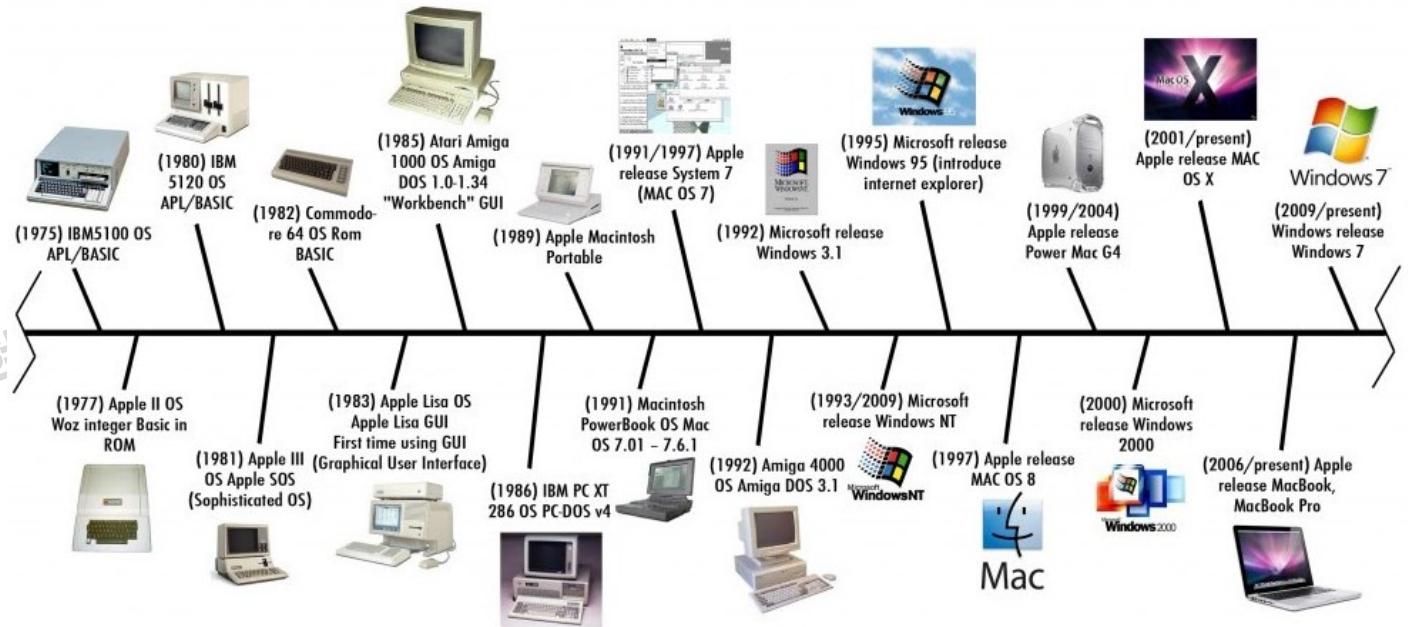


Classes of Computers

- Personal computers
 - General purpose, variety of software
 - Subject to cost/performance tradeoff
- Server computers
 - Network-based
 - High capacity, performance, reliability
 - Range from small servers to building-sized
- Supercomputers
 - High-end scientific and engineering calculations
 - Highest capability but represent a small fraction of the overall computer market
- Embedded computers
 - Hidden as components of systems
 - Stringent power/performance/cost constraints


The Post-PC Era

- Personal Mobile Device (PMD)
 - Battery operated
 - Connects to the Internet
 - Hundreds of dollars
 - Smartphones, tablets, electronic glasses
- Cloud computing
 - Warehouse Scale Computers (WSC)
 - Software as a Service (SaaS)
 - A portion of software runs on a PMD, and a portion runs in the Cloud
 - Amazon and Google
- Fog computing and edge computing involve pushing intelligence and processing capabilities down closer to where the data originates from pumps, motors, sensors, relays, etc.

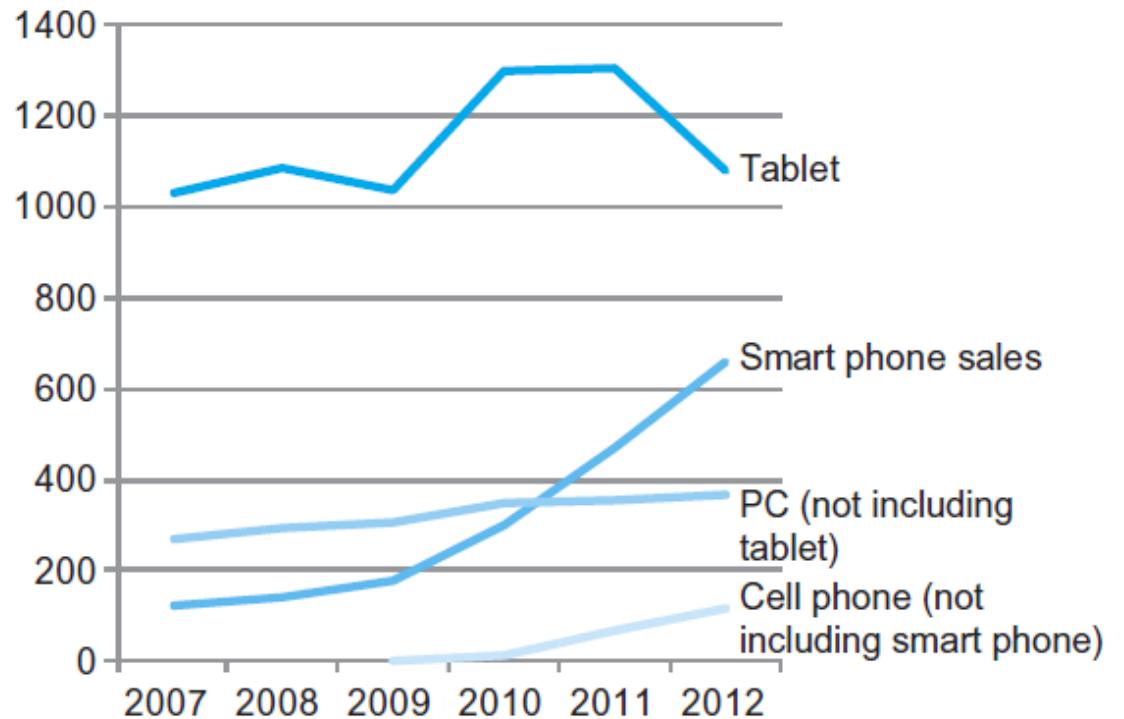


Exploring the Box (iMAC)

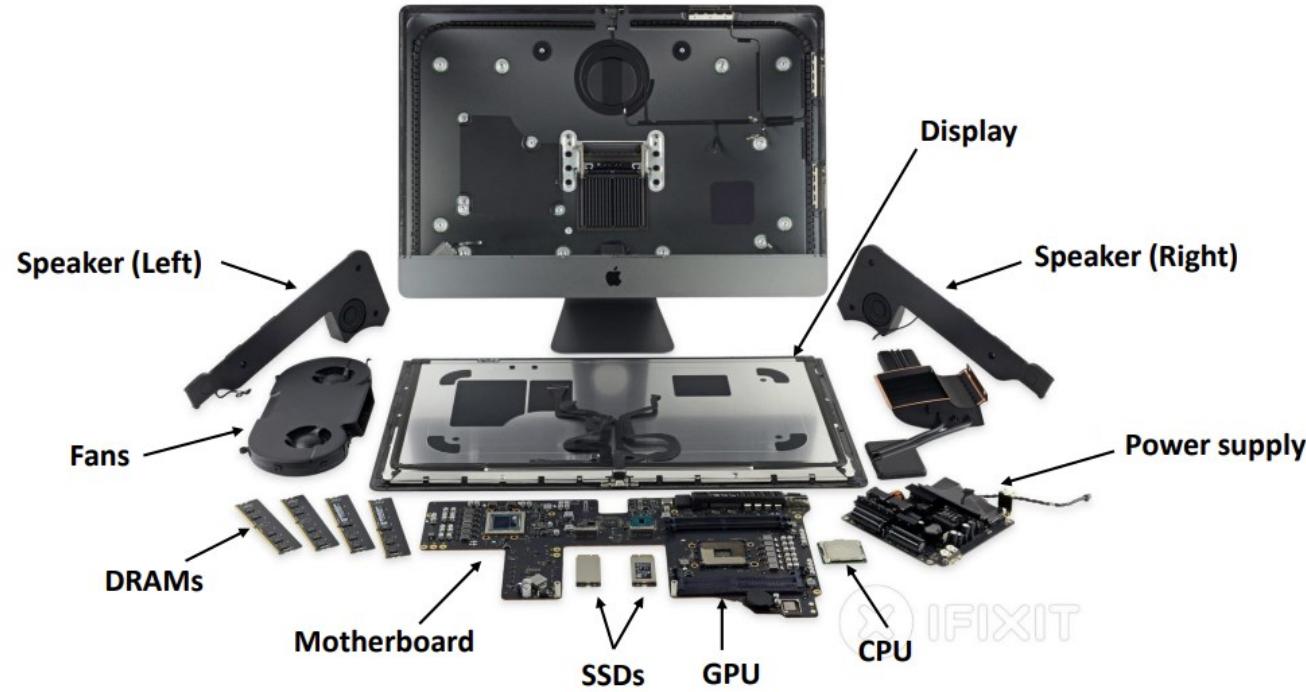- Central Processing unit (CPU), Graphical Processing Unit (GPU)
- Memory: DRAMs, SSD
- IO, Peripherals: Display, speaker




Von Neumann Architecture

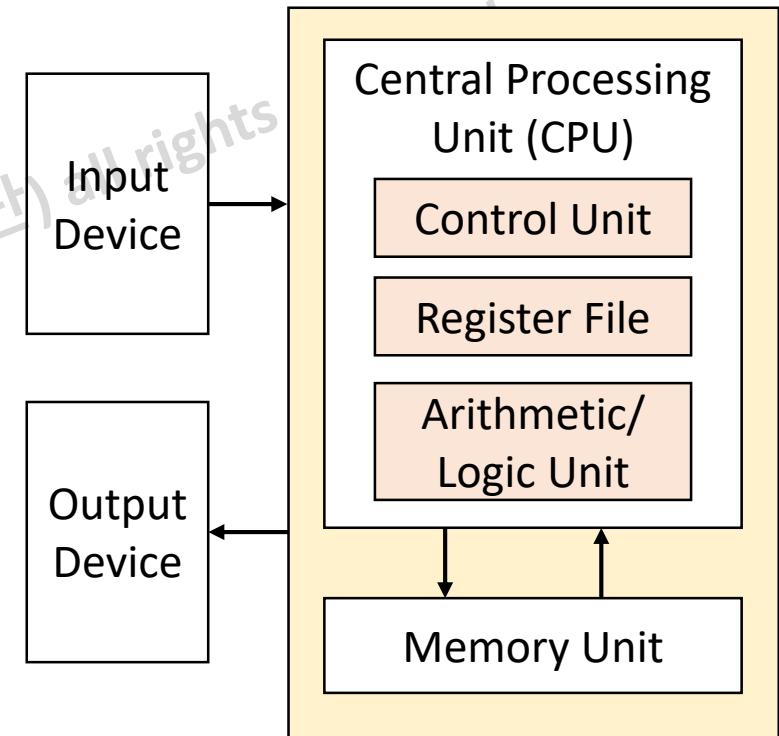- A design architecture for an electronic digital computer with these components:
 - A processing unit that contains an *arithmetic logic unit* (*ALU*) and processor registers
 - A control unit that contains an *instruction register* and *program counter*
 - Memory that stores data and instructions
 - External mass storage
 - Input and output mechanisms



Below Your Program

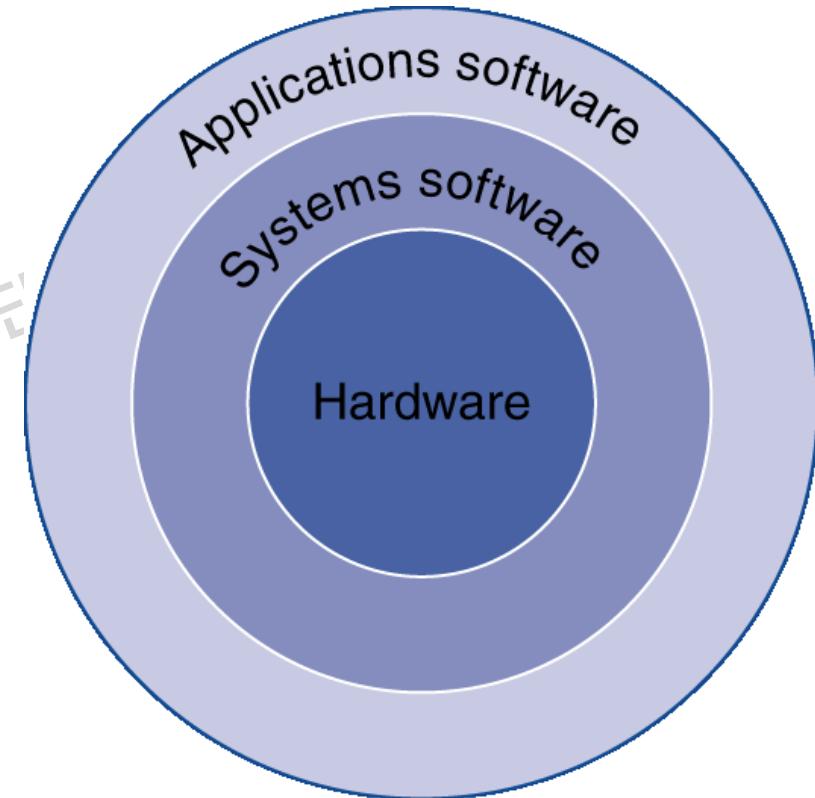- Application software
 - Written in high-level language (HLL)
- System software
 - Compiler: translates HLL code to machine code
 - Operating System: service code
 - Handling input/output
 - Managing memory and storage
 - Scheduling tasks & sharing resources
- Hardware
 - Processor, memory, I/O controllers



Levels of Program Code

- High-level language
 - Level of abstraction closer to problem domain
 - Provides for productivity and portability
- Assembly language
 - Textual representation of instructions
- Hardware representation
 - Binary digits (bits)
 - Encoded instructions and data

High-level
language
program
(in C)


```
swap(int v[], int k)
{int temp;
 temp = v[k];
 v[k] = v[k+1];
 v[k+1] = temp;
}
```

Assembly
language
program
(for RISC-V)

```
swap:
    sll1 x6, x11, 3
    add x6, x10, x6
    ld x5, 0(x6)
    ld x7, 8(x6)
    sd x7, 0(x6)
    sd x5, 8(x6)
    jalr x0, 0(x1)
```


Binary machine
language
program
(for RISC-V)
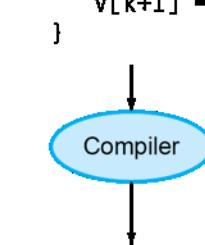
```
00000000001101011001001100010011
0000000000110010100000001100110011
0000000000000000110011001010000011
0000000000100001100110011001110000011
000000000011100110011000000100011
000000000010100110011010000100011
00000000000000001000000001100110011
```




Instruction Set Architecture (ISA)

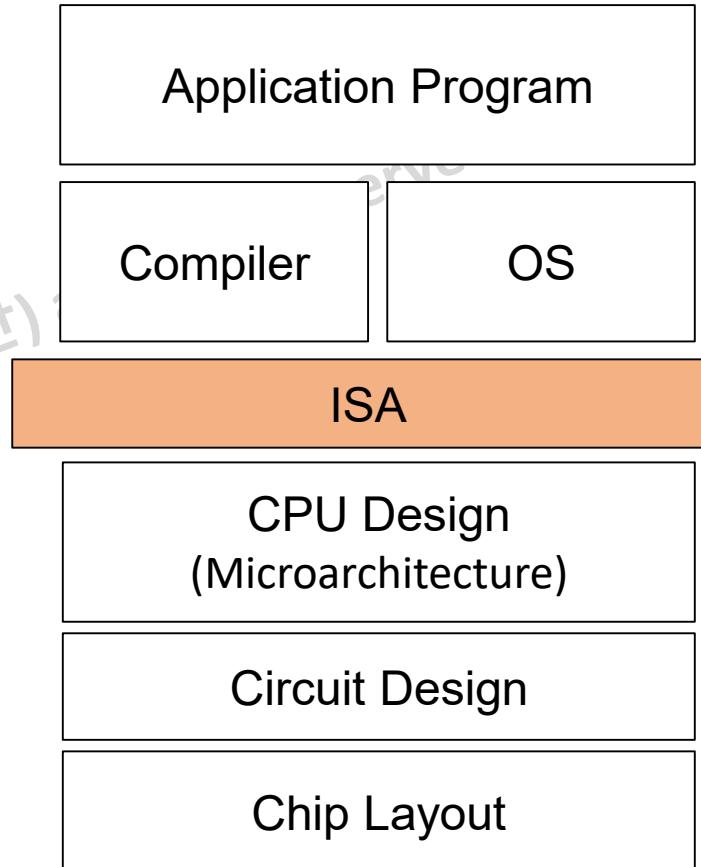- The repertoire of instructions of a computer
- Different computers have different instruction sets
 - But with many aspects in common
- Early computers had very simple instruction sets
 - Simplified implementation
 - Many modern computers also have simple instruction sets




Instruction Set Architecture (ISA)

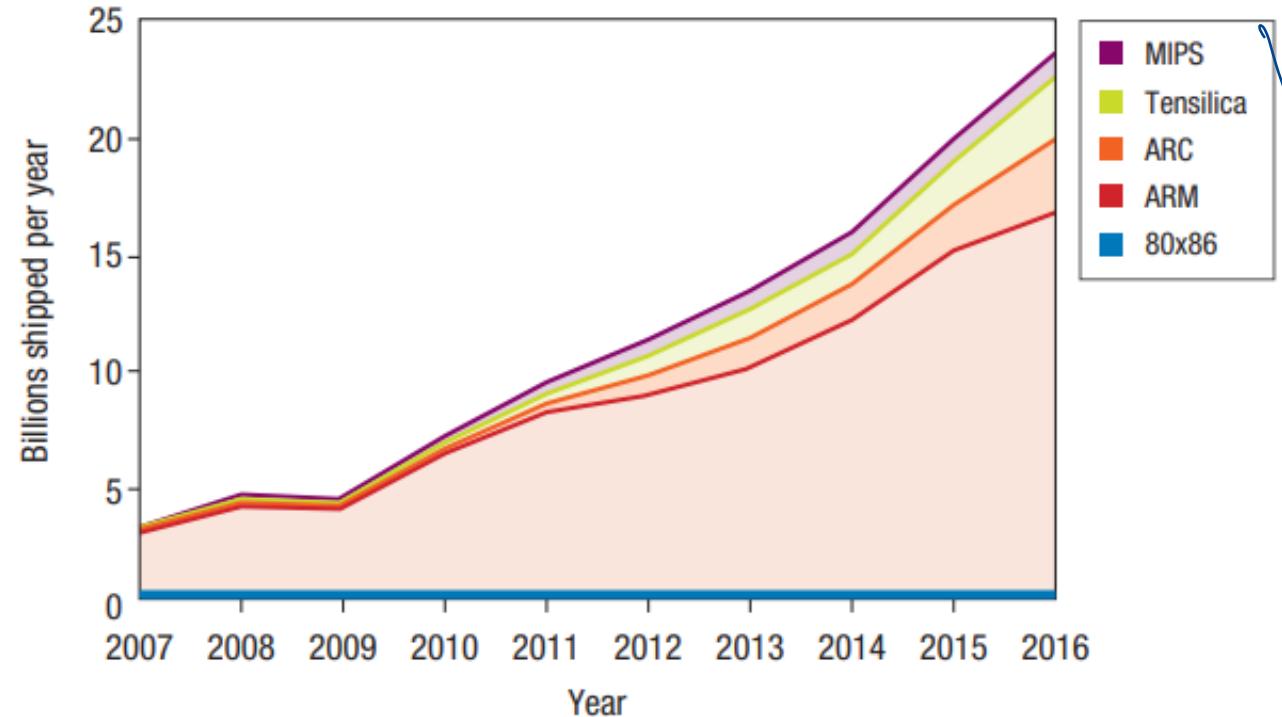- Most ISAs: X86, ARM, Power, MIPS, SPARC
 - Commercially protected by patents
 - Preventing practical efforts to reproduce the computer systems.



The RISC-V Instruction Set

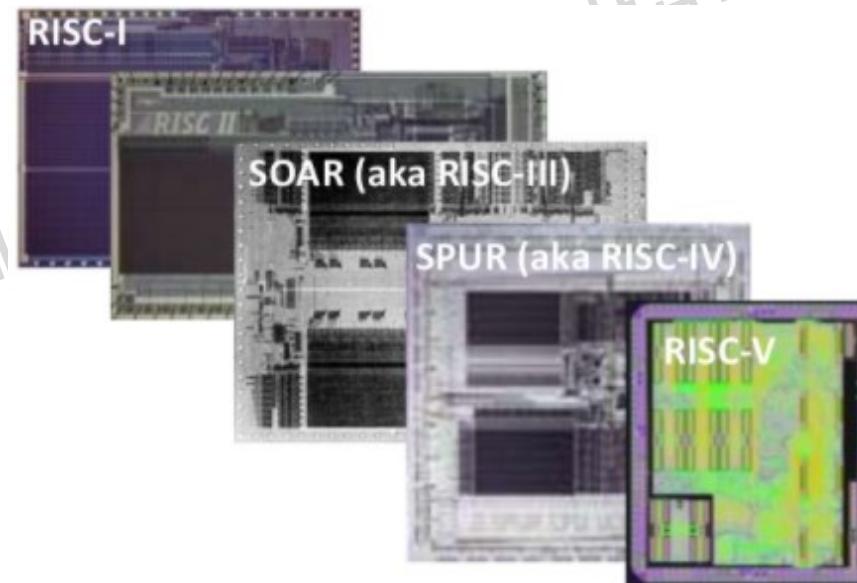- RISC-V (aka "risk-five"): Developed at UC Berkeley as open ISA
 - RISC-I (1981), RISC-II (1983), SOAR (1984), SPUR (1989), RISC-V (2010)
 - Now managed by the RISC-V Foundation (riscv.org)
 - Typical of many modern ISAs
- Similar ISAs have a large share of the embedded core market
 - Applications in consumer electronics, network/storage equipment, cameras, printers,...



RISC-V Ecosystem

- The RISC-V Foundation (www.riscv.org) was founded in 2015
- An open, collaborative community of S/W and H/W innovators based on the RISC-V ISA.



Source: <https://riscv.org/2019/05/getting-started-with-risc-v-china-roadshow-proceedings/ultrasoc-ppt/>

Why RISC-V is popular nowadays?

- Why RISC-V?
 - A **free and open** ISA
 - **Simple**: Far smaller than other commercial ISAs
 - **Clean-slate** design
 - Clear separation between user and privilege levels
 - Avoid micro-architecture or technology-specific details
 - A modular ISA
 - A small standard base ISA, i.e., RV32I
 - Multiple standard extensions
 - A two-page card for RISC-V
 - Instruction formats: 16/32/64/128-bit formats
 - Base integer instructions and extensions
 - Load/store
 - Shifts/arithmetic/logical/comparison
 - Branches/jump and link

Base Integer Instructions: RV32I, RV64I, and RV128I				RV Privileged Instructions			
Category	Name	Fmt	RV32I Base	+RV(64,128)	Category	Name	RV mnemonic
Loads	Load Byte	I	LB rd,r1,imm		CSR Access	Atomic R/W	CSSRRW rd,csr,rsl
	Load Halfword	I	LH rd,r1,imm			Atomic Read & Set Bit	CSSRRS rd,csr,rsl
	Load Word	I	LW rd,r1,imm			Atomic Read & Clear Bit	CSSRCR rd,csr,rsl
	Load Byte Unsigned	I	LBU rd,r1,imm			Atomic R/W Imm	CSSRWR1 rd,csr,imm
Load Half Unsigned		I	LHU rd,r1,imm			Atomic Read & Set Imm	CSSRRI1 rd,csr,imm
		I	L(W)U rd,r1,imm			Atomic Read & Clear Imm	CSSRCRI1 rd,csr,imm
		S	SB rs1,r2,imm			Change Level	ECALL
Stores	Store Byte	S	SB rs1,r2,imm		Environment	Breakpoint	EBREAK
	Store Halfword	S	SH rs1,r2,imm			Return	ERET
	Store Word	S	SW rs1,r2,imm			Trap Redirection	MRTB
Shifts	Shift Left	R	SLL rd,r1,r2		Redirect Trap to Supervisor	Redirection	MRTB
	Shift Left Immediate	I	SLLI rd,r1,shamt			Hypervisor Trap to Supervisor	HRTB
	Shift Right	R	SRL rd,r1,r2			Interrupt	WF1
	Shift Right Immediate	I	SRLI rd,r1,shamt			MMU	Supervisor FENCE SFENCE.VM rsl
Shift Right Arithmetic		R	SRRA rd,r1,r2				
		I	SRRAI rd,r1,shamt				
Arithmetic	ADD	R	ADD rd,r1,r2		Optional Compressed (16-bit) Instruction Extension: RVC		
	ADD Immediate	I	ADDI rd,r1,imm		Category	Name	Fmt
	SUBtract	R	SUB rd,r1,r2			RVC	
	Load Upper Imm	U	LUI rd,imm			RV equivalent	
Add Upper Imm to PC	UI	UIPC rd,imm					
Logical	XOR	R	XOR rd,r1,r2		Loads	Load Word	CL
	XOR Immediate	I	XORI rd,r1,imm			Load Word SP	CL
	OR	R	OR rd,r1,r2			Load Double	CL
	OR Immediate	I	ORI rd,r1,imm			Load Double SP	CL
AND	AND	R	AND rd,r1,r2			Load Quad	CL
	AND Immediate	I	ANDI rd,r1,imm			Load Quad SP	CL
Compare	Set <	R	SLT rd,r1,r2		Stores	Store Word	CL
	Set < Immediate	I	SLTI rd,r1,imm			Store Word SP	CL
	Set < Unsigned	R	SLTU rd,r1,r2			Store Double	CL
	Set < Imm Unsigned	I	SLTUI rd,r1,imm			Store Double SP	CL
Branches	Branch =	SB	BEQ r1,r2,imm		Store Quad	Store Quad	CL
	Branch =	SB	BNE r1,r2,imm			Store Quad SP	CL
	Branch <	SB	BLT r1,r2,imm				
	Branch >	SB	BGE r1,r2,imm				
Branch < Unsigned	Branch < Unsigned	SB	BLTU r1,r2,imm				
	Branch > Unsigned	SB	BGEU r1,r2,imm				
Jump & Link	JAL	U	JAL rd,imm				
	Jump & Link Register	U	JALR rd,r1,imm				
Sync	Synch Thread	I	FENCE				
	Synch Instr & Data	I	FENCE.I				
System	System CALL	I	SCALL				
	System BREAK	I	SBREAK				
Counters	Read CYCLE	I	RDCYCLE rd		Arithmetic	ADD	CR
	Read CYCLE upper Half	I	RD CYCLEH rd			ADD Immediate	CR
Read TIME	Read TIME	I	RDTIME rd			ADD Word Imm	CR
	Read TIME upper Half	I	RD TIMEH rd			ADD SP Imm * 16	CR
Read INSTR RETired	Read INSTR RETired	I	RDINSTRUCTION rd			Load Immediate	CI
	Read INSTR upper Half	I	RD INSTRUCTIONH rd			Load Upper Imm	CI
Shifts	Shift Left Imm	CI	SILLI rd,imm			MoVe	CR
	Branch+0	CI	BEQZ r1,imm			SUB	CR
	Branch+0	CI	CBNEZ r1,imm				
		CI	BR r1,imm				
Jump	Jump	CI	J r1		Shifts	Shift Right Imm	CI
	Jump Register	CI	JAL r1,imm			BEQ r1',x0,imm	CI
Jump & Link	JAL	CI	JAL r1,imm			BNE r1',x0,imm	CI
	Jump & Link Register	CI	JALR r1,imm				
System	Env. BREAK	CI	EBREAK				
		CI	ESBREAK				
32-bit Instruction Formats							
31	30	25-24	21-20	19	15-14	12-11	8-7
R	I	funct7	rs2	rsl	funct3	rd	opcode
I	S	imm[11:0]	rs2	rsl	funct3	rd	opcode
S	SB	imm[11:5]	rs2	rsl	funct3	imm[4:0]	opcode
SB	SB	imm[12] imm[10:5]	rs2	rsl	funct3	imm[4:1] imm[1]	opcode
SB	SB	imm[12]	imm[11:2]	imm[11]	imm[19:12]	rd	opcode
SB	UJ	imm[20]	imm[10:1]	imm[11]	imm[19:12]	rd	opcode
16-bit (RVC) Instruction Formats							
15	14	11-10	9-8	7-6	5-4	3-2	1-0
R	I	funct4	rd/rsl	rs2	imm	op	
I	S	funct3	imm	rd	imm	op	
S	SS	funct3	imm	rd	imm	op	
SS	CTW	funct3	imm	rd	op		
CTW	CL	funct3	imm	rs1'	imm	rd	
CL	CS	funct3	imm	rs1'	imm	rd	
CS	CB	funct3	offset	rs1'	imm	rd	
CB	CI	funct3	jump target	rs1'	imm	op	

RISC-V Integer Base (RV32I/64I/128I), privileged, and optional compressed extension (RVC). Registers x1-x31 and the pc are 32 bits wide in RV32I, 64 in RV64I, and 128 in RV128I ($x=0-6$). The RV1 base of <50 classic integer RISC instructions is retained. Every 16-bit RVC instruction matches an existing 32-bit RV1 instruction. See [risc.org](#).

Example: Arithmetic Operations

- Add and subtract, three operands
 - Two sources and one destination
- add a, b, c // a gets b + c
- All arithmetic operations have this form
- *Design Principle 1:* Simplicity favors regularity
 - Regularity makes implementation simpler
 - Simplicity enables higher performance at lower cost

$$a = b + c$$

if you give
add(a, b, c)

Arithmetic example

- C code:

$$f = (g + h) - (i + j);$$

- Compiled RISC-V code:

```
add t0, g, h      // temp t0 = g + h
```

```
add t1, i, j      // temp t1 = i + j
```

```
add f, t0, t1     // f = t0 - t1
```

$t_0 + t_1$

$t_0 + t_1$

$f = t_0 - t_1$

Register Operands

- Arithmetic instructions use register operands
- RISC-V 32I has a $32 \times 32\text{-bit}$ register file
 - Use for frequently accessed data
 - 32-bit data is called a “word”
 - $32 \times 32\text{-bit}$ general purpose registers x_0 to x_{31}
 - 32-bit data is called a “word”
- *Design Principle 2:* Smaller is faster
 - c.f. main memory: millions of locations

RISC-V register

- x0: the constant value 0
- x1: return address
- x2: stack pointer
- x3: global pointer
- x4: thread pointer
- x5 – x7, x28 – x31: temporaries
- x8: frame pointer
- x9, x18 – x27: saved registers
- x10 – x11: function arguments/results
- x12 – x17: function arguments

Register Operand Example

- C code:

$f = (g + h) - (i + j);$


- Variables f, ..., j are in x19, x20, ..., x23

- Compiled RISC-V code:

add t0, g, h // temp t0 = g + h

add t1, i, j // temp t1 = i + j

add f, t0, t1 // f = t0 - t1

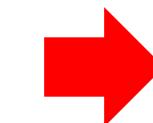

add x5, x20, x21

add x6, x22, x23

sub x19, x5, x6

Road map


Introduction to RISC-V

Verilog HDL
Dataflow modelling

Labs

Dataflow modelling

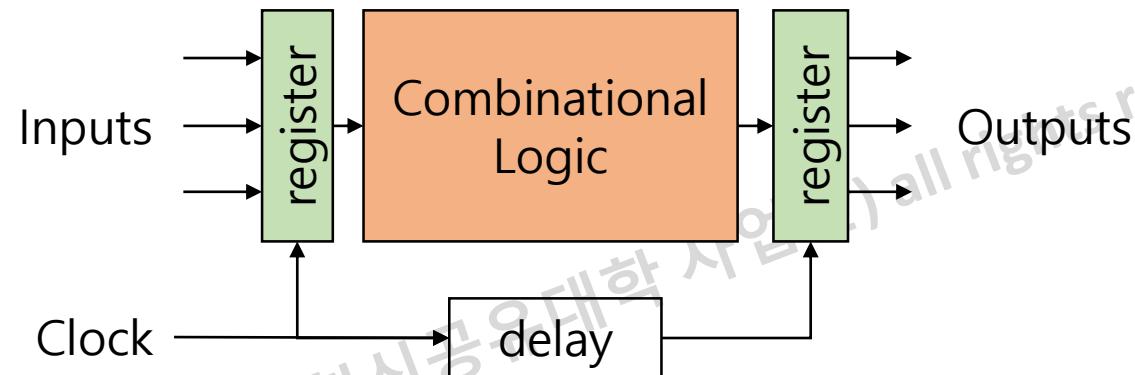- Any digital system can be constructed by *interconnecting registers and a combinational logic* put between them for performing the necessary functions.



- Dataflow provides a powerful way to implement a design.
- Logic synthesis tools can be used to create a gate-level circuit from a dataflow design description.
- RTL (register transfer level) is a combination of dataflow and behavioral modeling.

Assignments

- Two basic forms of assignments
 - Continuous assignment: assign values to **nets**
 - Procedural assignment: assign values to **variables**
- Two additional forms of assignments: procedural continuous assignments
 - **assign/deassign**
 - **force/release**
- An assignment consists of two parts:
 - a left-hand side (LHS) and a right-hand side (RHS) separated by = or <=
 - RHS: any expression that evaluates to a value to which the LHS value is to be assigned.
 - LHS: can take one of the forms given on the **Next** page.

Assignments

Table 6-1—Legal left-hand forms in assignment statements

Statement type	<i>↑ kinda like constant</i>	Left-hand side
Continuous assignment		Net (vector or scalar) Constant bit-select of a vector net Constant part-select of a vector net Constant indexed part-select of a vector net Concatenation or nested concatenation of any of the above left-hand side
Procedural assignment		Variables (vector or scalar) Bit-select of a vector reg, integer, or time variable Constant part-select of a vector reg, integer, or time variable Indexed part-select of a vector reg, integer, or time variable Memory word Concatenation or nested concatenation of any of the above left-hand side

Continuous Assignments

- Continuous assignment: the most basic statement of dataflow modeling.
 - It is used to drive a value onto a net.
 - It is always active.
 - Provides a way to model combinational logic without specifying an interconnection of gates. Instead, it specifies the logical expression that drives the net.
 - It can only update values of net data types such as wire, triand, etc.
 - This assignment shall occur whenever the value of the right-hand side changes.
- Example:

```
assign {c_out, sum[3:0]} = a[3:0] + b[3:0] + c_in;
```

Continuous Assignments

- A continuous assignment begins with the keyword assign.

```
assign net_lvalue = expression;
```

```
assign net1 = expr1,  
       net2 = expr2,  
       ...,  
       netn = exprn;
```

- net_lvalue is a scalar or vector net or their concatenation.
- RHS operands can be variables or nets, or function calls.
- Registers or nets can be scalar or vectors.
- Delay values can be specified.

all rights reserved.

Continuous Assignments

- An implicit continuous assignment
 - is the shortcut of declaring a net first and then writing a continuous assignment on the net.
 - is always active.
 - can only have one implicit declaration assignment per net.

```
wire out;           // net declaration  
assign out = in1 & in2; // regular continuous assignment  
  
wire out = in1 & in2; // implicit continuous assignment
```

Copyright 20

Data types

- Two classes of data types:
 - **nets**: Nets mean any hardware connection points.
 - **variables**: Variables represent any data storage elements.
- Variable data types
 - reg
 - integer
 - time
 - real
 - realtime

Variable data types

- A reg variable
 - holds a value between assignments.
 - may be used to model hardware registers.
 - need not actually represent a hardware storage element.

```
reg a, b;          // reg a, and b are 1-bit reg  
reg [7:0] data_a; // an 8-bit reg, the msb is bit 7  
reg [0:7] data_b; // an 8-bit reg, the msb is bit 0  
reg signed [7:0] d; // d is an 8-bit signed reg
```

- The integer variable
 - contains integer values.
 - has at least 32 bits.
 - is treated as a signed reg variable with the least-significant bit (LSB) being bit 0.

```
integer i,j;      // declare two integer variables  
integer data[7:0]; // array of integer
```

The time, real, and realtime variables

- The time variable

- is used for storing and manipulating simulation time quantities.
- is typically used in conjunction with the \$time system task.
- holds only unsigned value and is at least 64 bits, with the LSB being bit 0.

```
time events;      // hold one time value  
time current_time; // hold one time value
```

- The real and realtime variables

- cannot use range declaration and their initial values are defaulted to zero (0.0).

```
real events;          // declare a real variable  
realtime current_time; // hold current time as| real
```

Vectors

- A vector (multiple bit width) describes a bundle of signals as a basic unit.
 - [high:low] or [low:high]
 - The leftmost bit is the MSB.
 - Both nets and reg data types can be declared as vectors.
- The default is 1-bit vector or called scalar.
- Bit-Select and Part-Select
 - integer and time can also be accessed by bit-select or part-select.
 - real and realtime are not allowed to be accessed by bit-select or part-select.
 - Constant part select: data_bus[3:0], bus[3]
 - Variable part select:
 - [<starting_bit> +:width]: data_bus[8+:8]
 - [<starting_bit> -:width]: data_bus[15:-8]

Array and memory elements

- Array and Memory Elements
 - all net and variable data types are allowed to be declared as **multi-dimensional** arrays.
 - an array element can be a scalar or a vector if the element is a net or reg data type.

```
wire a[3:0];          // a scalar wire array of 4 elements
reg d[7:0];           // a scalar reg array of 8 elements
wire [7:0] x[3:0];    // an 8-bit wire array of 4 elements
reg [31:0] y[15:0];   // a 32-bit reg array of 16 elements
integer states [3:0]; // an integer array of 4 elements
time   current[5:0];  // a time array of 6 elements
```


Bitwise operations

- Bitwise operators
 - They perform a bit-by-bit operation on two operands.
 - A z is treated as x in bit-wise operation.
 - The shorter operand is zero-extended to match the length of the longer operand.

Symbol	Operation
\sim	Bitwise negation
$\&$	Bitwise and
$ $	Bitwise or
$^$	Bitwise exclusive or
$\sim\wedge, \wedge\sim$	Bitwise exclusive nor

Example: 4-to-1 MUX

```
module mux41_dataflow(i0, i1, i2, i3, s1, s0, out);
// Port declarations
input i0, i1, i2, i3;
input s1, s0;
output out;
// Using basic and, or , not logic operators.
assign out = (~s1 & ~s0 & i0) |
            (~s1 & s0 & i1) |
            (s1 & ~s0 & i2) |
            (s1 & s0 & i3);
endmodule
```

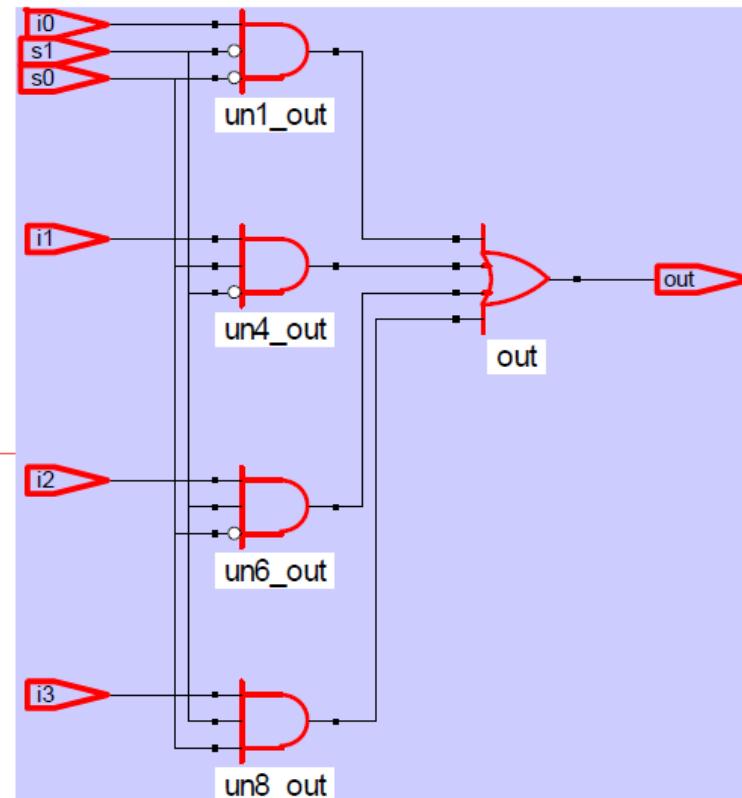

Copyright

Arithmetic Operators

- Arithmetic operators
 - If any operand bit has a value x, then the result is x.
 - The operators + and – can also be used as unary operators to represent signed numbers.
 - Modulus operators produce the remainder from the division of two numbers.
 - In Verilog HDL, 2's complement is used to represent negative numbers.

Symbol	Operation
+	Addition
-	Subtraction
*	Multiplication
/	Division
**	Exponent (power)
%	Modulus

Concatenation and Replication operations


- Concatenation operators
 - The operands must be sized.
 - Operands can be scalar nets or registers, vector nets or registers, bit-select, part-select, or sized constants.
 - Example: $y = \{a, b[0], c[1]\};$
- Replication operators
 - They specify how many times to replicate the number inside the braces.
 - Example: $y = \{a, 4\{b[0]\}, c[1]\};$

Symbol	Operation
{ , }	Concatenation
{const_expr{}}	Replication

Example: A 4-bit two's complement adder

```
module twos_adder(x, y, c_in, sum, c_out);
// I/O port declarations
input [3:0] x, y; // declare as a 4-bit array
input c_in;
output [3:0] sum; // |declare as a 4-bit array
output c_out;
wire [3:0] t; // outputs of xor gates

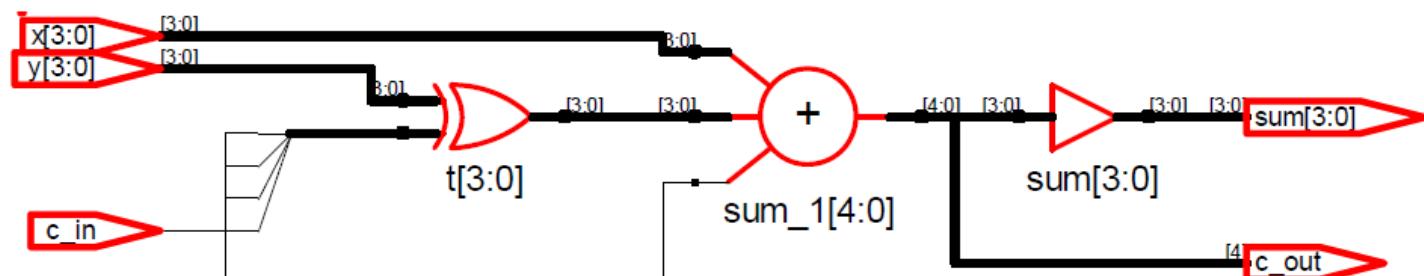// Specify the function of a two's complement adder
assign t = y ^ {4{c_in}};
assign {c_out, sum} = x + t + c_in;
endmodule
```




Reduction operators

- Reduction operators
 - perform only on one vector operand.
 - carry out a bit-wise operation on a single vector operand and yield a 1-bit result.
 - work bit by bit from right to left.

Symbol	Operation
$\&$	Reduction and
$\sim\&$	Reduction nand
$ $	Reduction or
$\sim $	Reduction nor
$^$	Reduction exclusive or
$\sim^, \sim\sim$	Reduction exclusive nor

Example: An All-Bit-Zero/One detector

```
module all_bit_01_detector_reduction(x, zero, one);
// I/O port declarations
input [7:0] x;
output zero, one;
// dataflow modeling
assign zero = ~(|x); // all-bit zero detector
assign one = &x;      // all-bit one detector
endmodule
```

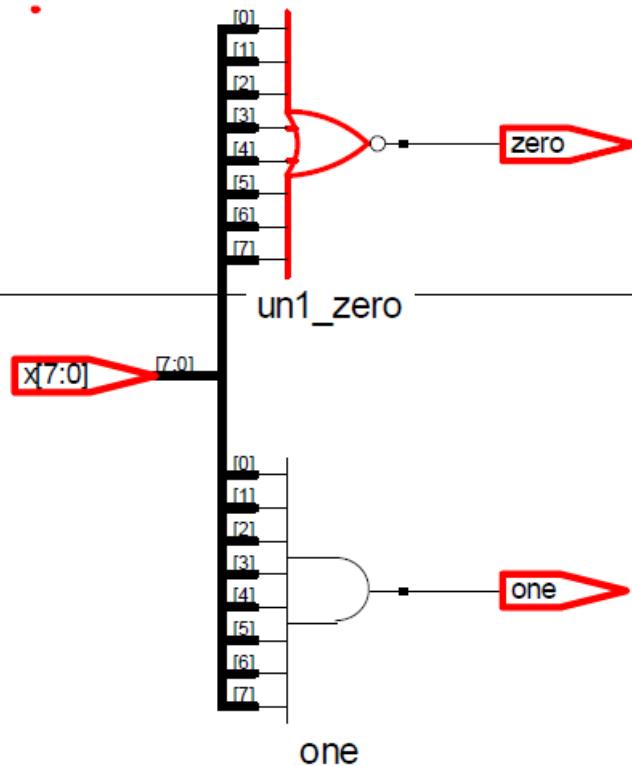

Copyri

Logical, relational Operators

- Logical operators
 - They always evaluate to a 1-bit value, 0, 1, or x.
 - If any operand bit is x or z, it is equivalent to x and treated as a false condition by simulators.

Symbol	Operation
!	Logical negation
&&	Logical and
	Logical or

- Relational operators
 - They return logical value 1 if the expression is true and 0 if the expression is false.
 - The expression takes a value x if there are any unknown (x) or z bits in the operands.


Symbol	Operation
>	Greater than
<	Less than
>=	Greater than or equal
<=	Less than or equal

Equality operations

- Equality operators
 - compare the two operands bit by bit, with zero filling if the operands are of unequal length.
 - return logical value 1 if the expression is true and 0 if the expression is false.
- The operators `(==, !=)` yield an x if either operand has x or z in its bits.
- The operators `(==:, !==:)` yield a 1 if the two operands match exactly and 0 if the two operands not match exactly.

Symbol	Operation
<code>==</code>	Logical equality
<code>!=</code>	Logical inequality
<code>==:</code>	Case equality
<code>!==:</code>	Case inequality

Example: A 4-b Magnitude Comparator

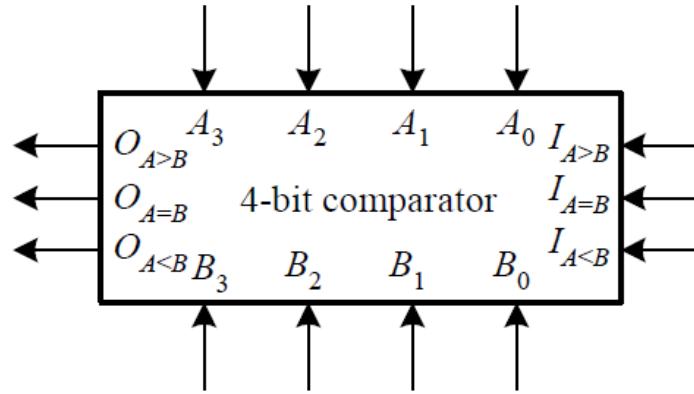

```
module four_bit_comparator(Iagt, Iaeq, Ialt, a, b, Oagt, Oaeq, Oalt);
// I/O port declarations
input [3:0] a, b;
input Iagt, Iaeq, Ialt;
output Oagt, Oaeq, Oalt;
// dataflow modeling using relation operators
assign Oaeq = (a == b) && (Iaeq == 1); // equality
assign Oagt = (a > b) || ((a == b)&& (Iagt == 1)); // greater than
assign Oalt = (a < b) || ((a == b)&& (Ialt == 1)); // less than
endmodule
```

Shift operators

- Logical shift operators
 - `>>` operator: logical right shift
 - `<<` operator: logical left shift
 - The vacant bit positions are filled with zeros.
- Arithmetic shift operators
 - `>>>` operator: arithmetic right shift
 - The vacant bit positions are filled with the MSBs (sign bits).
 - `<<<` operator: arithmetic left shift
 - The vacant bit positions are filled with zeros.

Symbol	Operation
<code>>></code>	Logical right shift
<code><<</code>	Logical left shift
<code>>>></code>	Arithmetic right shift
<code><<<</code>	Arithmetic left shift

Example: Shift operators

```
// example to illustrate logic and arithmetic shifts
module arithmetic_shift(x,y,z);
input signed [3:0] x;
output [3:0] y;
output signed [3:0] z;
assign y = x >> 1; // logical right shift
assign z = x >>> 1; // arithmetic right shift
endmodule
```

Note that: net variables x and z must be declared with the keyword `signed`.
Replaced net variable with `unsigned` net (i.e., remove the keyword `signed`)
and see what happens.

The Conditional Operator

- Conditional Operator


Usage: condition_expr ? true_expr: false_expr;

- The condition_expr is evaluated first.
- If the result is true then the true_expr is executed; otherwise the false_expr is evaluated.
 - if (condition_expr) true_expr;
 - else false_expr;
- a 2-to-1 multiplexer

```
assign out = selection ? in_1: in_0;
```

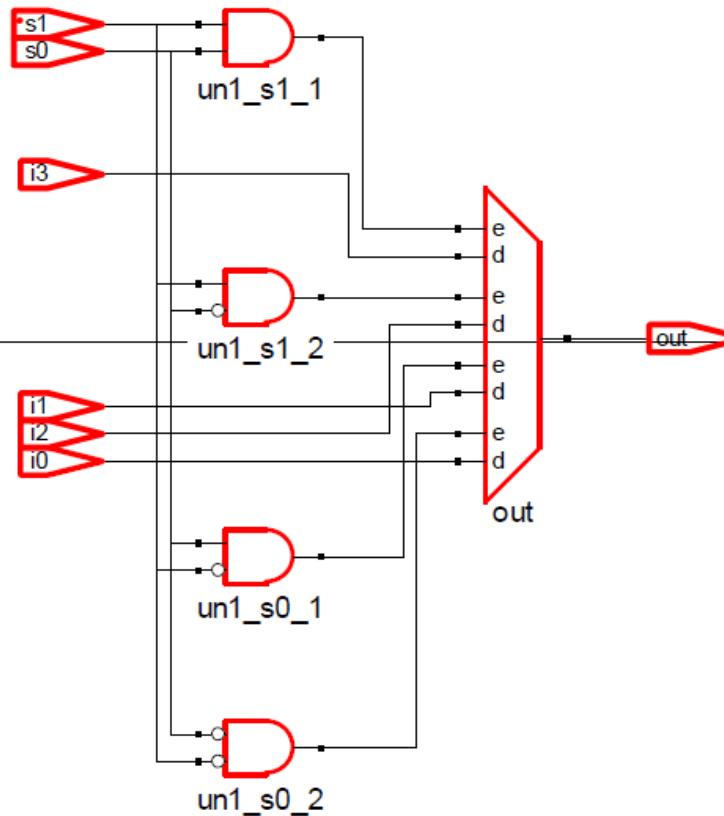Example: A 4-to-1 MUX

```
module mux4_to_1_cond (i0, i1, i2, i3, s1, s0, out);
// Port declarations from the I/O diagram
input  i0, i1, i2, i3;
input  s1, s0;
output out;
// Using conditional operator (?:)
assign out = s1 ? ( s0 ? i3 : i2 ) : (s0 ? i1 : i0) ;
endmodule
```



Copyright

Road map

Introduction to RISC-V

Verilog HDL
Dataflow modelling

Labs


Lab 1: Register file

- Lab 1: Design Register file
 - Implement a register file module
 - Create a test bench
 - Run simulation
 - Show the output result


Copyright 2022. (차세대반도체 혁신공유대학 사업단) all rights reserved.

Register file (riscv_regfile.v)

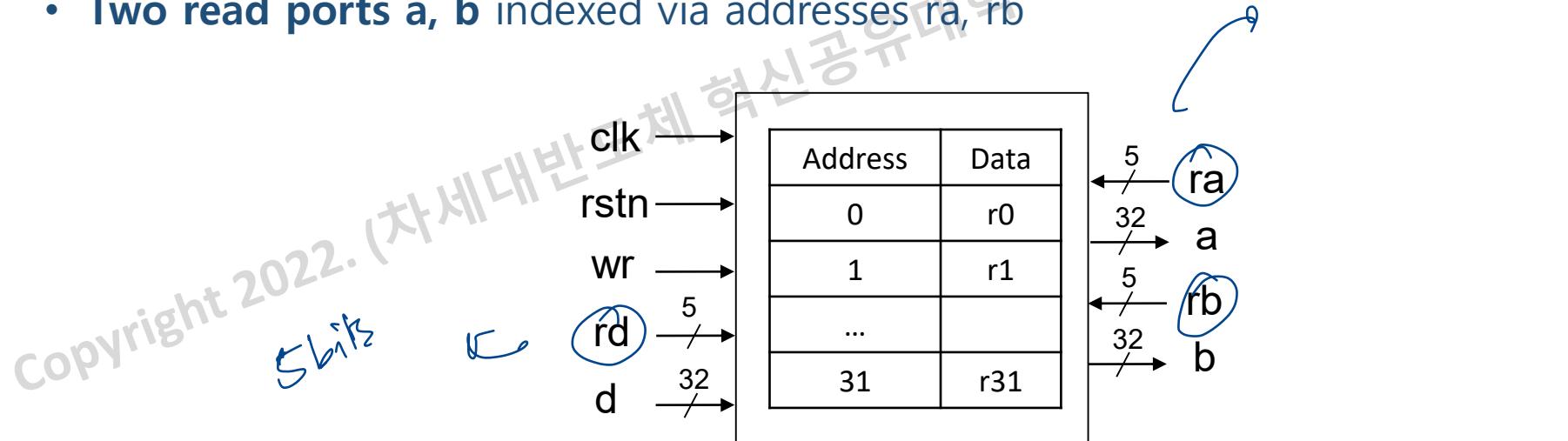- Keep frequently-used data
- Architecture: RF consist of 32 registers, 32-bits each
 - Numbered from 0 to 31
 - Can be referred by number: r0, r1, ..., r31
- Interface
 - **One write port d** indexed via an address rd
 - On falling edge when wr = 1
 - **Two read ports a, b** indexed via addresses ra, rb




Clock and reset ports (riscv_regfile.v)

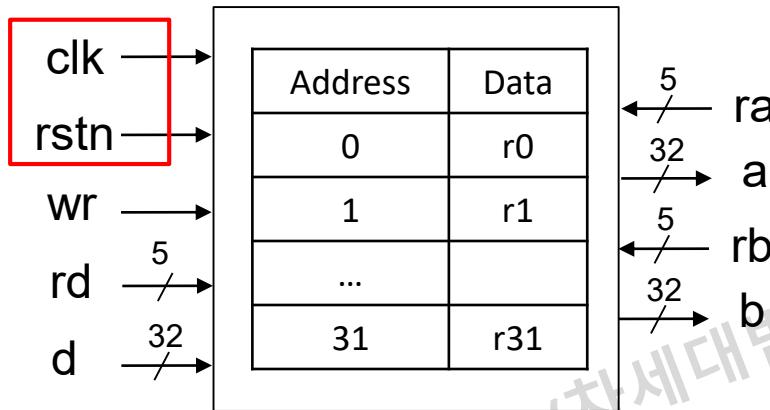

```
module riscv_regfile      ** Input / output ports definition
(
    input  clk_i           : module input/output could be connected to the other module
    ,input  rstn_i          : Input controlled by designer testbench for simulation.
                           : output monitored by testbench for functional verification.

    ,input [ 31:0] rd0_value_i // data to write
    ,input [ 4:0]  rd0_i      // address to write
    ,input        wr         // write enable signal
    ,input [ 4:0]  ra0_i      // address to read
    ,input [ 4:0]  rb0_i      // address to read
    ,output [ 31:0] ra0_value_o // read data from address ra0_i
    ,output [ 31:0] rb0_value_o // read data from address rb0_i
);
```


Write ports (riscv_regfile.v)

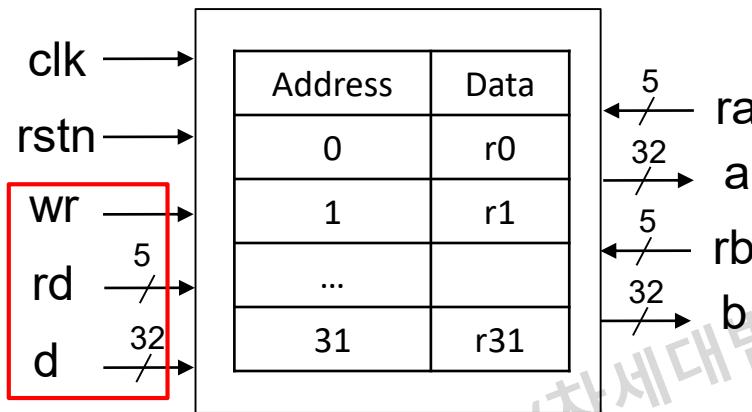

```
module riscv_regfile      ** Input / output ports definition
(
    : module input/output could be connected to the other module
    : Input controlled by designer testbench for simulation.
    : output monitored by testbench for functional verification.

    input  clk_i
    ,input  rstn_i
    ,input [ 31:0] rd0_value_i // data to write
    ,input [ 4:0]  rd0_i      // address to write
    ,input        wr         // write enable signal
    ,input [ 4:0]  ra0_i     // address to read
    ,input [ 4:0]  rb0_i     // address to read
    ,output [ 31:0] ra0_value_o // read data from address ra0_i
    ,output [ 31:0] rb0_value_o // read data from address rb0_i
);
```


Read ports (riscv_regfile.v)

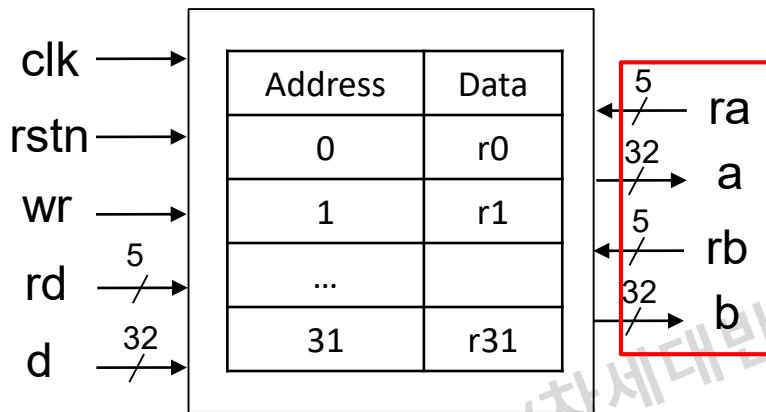

```
module riscv_regfile      ** Input / output ports definition
(
    : module input/output could be connected to the other module
    : Input controlled by designer testbench for simulation.
    : output monitored by testbench for functional verification.

    input  clk_i
    ,input  rstn_i
    ,input [31:0] rd0_value_i // data to write
    ,input [4:0]  rd0_i      // address to write
    ,input       wr        // write enable signal
    ,input [4:0]  ra0_i     // address to read
    ,input [4:0]  rb0_i     // address to read
    ,output [31:0] ra0_value_o // read data from address ra0_i
    ,output [31:0] rb0_value_o // read data from address rb0_i
);
```

Internal signals (riscv_regfile.v)

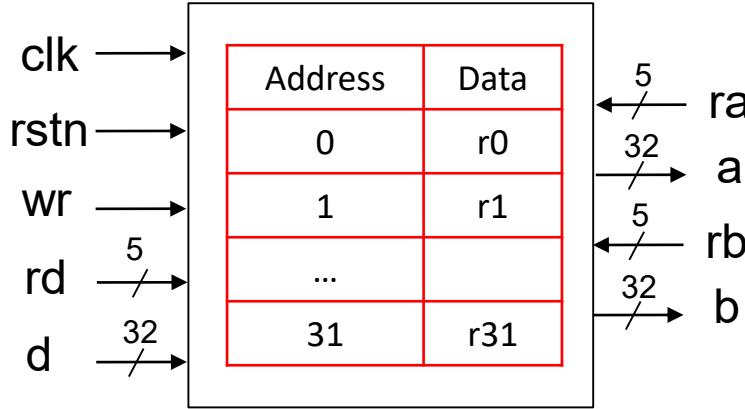

```
reg [31:0] reg_r1_q;  
reg [31:0] reg_r2_q;  
...  
reg [31:0] reg_r31_q;  
  
wire [31:0] x0_zero_w = 32'b0;  
wire [31:0] x1_ra_w = reg_r1_q;  
...  
wire [31:0] x31_t6_w = reg_r31_q;
```


internally used registers definition

wire assignments using different names

#	Name	Usage
r0	zero	Hard-wired zero
r1	ra	Return address
r2	sp	Stack pointer
r3	gp	Global pointer
r4	tp	Thread pointer
r5~r7	t0~t2	Temporaries (Caller-save registers)
r8	s0/fp	Saved registers/ Frame pointer
r9	s1	Saved registers
r10~r17	a0~a8	Function arguments
r18~r26	s2~s11	Temporaries (Caller-save registers)
r28~r31	t3~t6	Temporaries (Caller-save registers)


Write operation

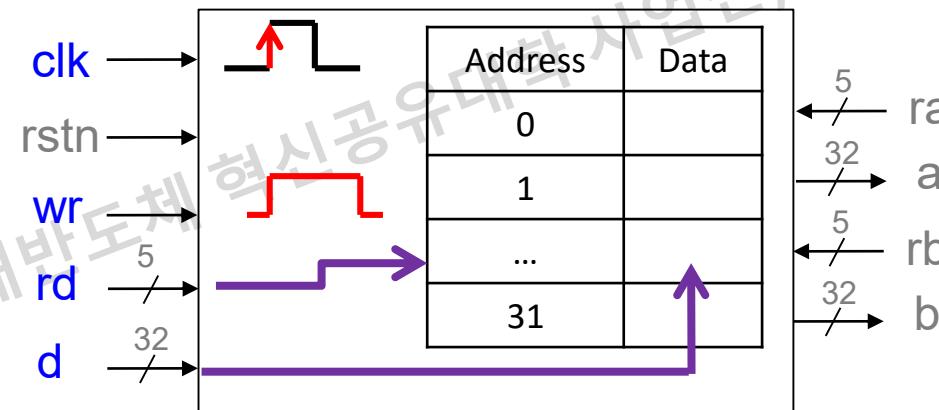- Sequential logic
- Pseudocode
 - If $wr == 1 \ \&\& \$ positive edge of clk
 - $\text{regs}[rd] \leftarrow d$



Write operation (riscv_regfile.v)

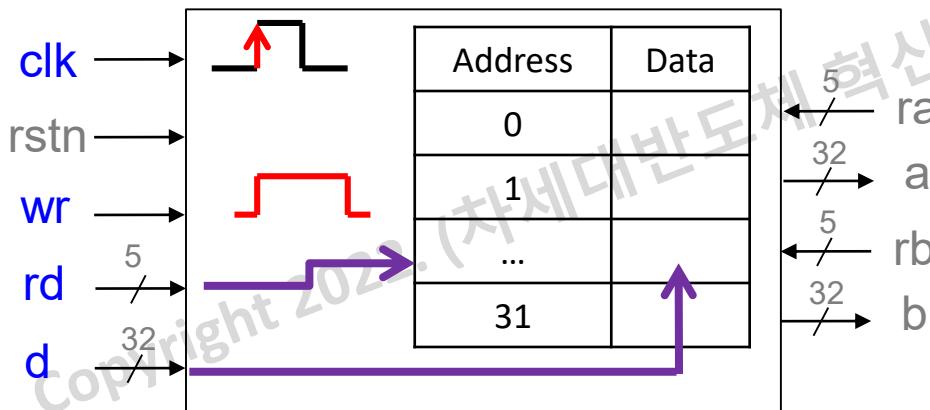- Use an “always” block to represent write operations
 - Reset: assign a register to “0”
 - Use “if”
 - To check the write enable flag
 - To check the register address




```
always @ (posedge clk_i or negedge rstn_i) begin
    if (~rstn_i) begin
        reg_r1_q    <= 32'h00000000;
        reg_r2_q    <= 32'h00000000;
        ...
        reg_r31_q   <= 32'h00000000;
    end
    else begin
        if (wr) begin
            if (rd0_i == 5'd1) reg_r1_q <= rd0_value_i;
            if (rd0_i == 5'd2) reg_r2_q <= rd0_value_i;
            ...
            if (rd0_i == 5'd31) reg_r31_q <= rd0_value_i;
        end
    end
end
end
```

reset value “0” for initialization

write 32bits new data to new address when write enabled


Read operation (riscv_regfile.v)

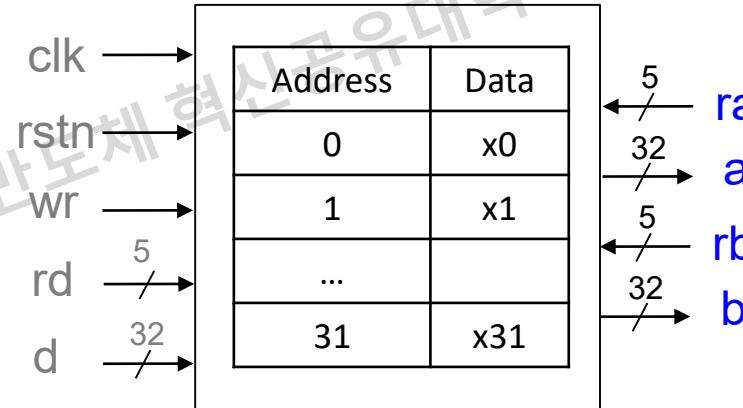- Combinational Logic
- Pseudocode
 - Input: addresses ra and rb
 - Internal signals: regs[0:31]
 - Output
 - $a \leftarrow \text{regs}[ra]$
 - $b \leftarrow \text{regs}[rb]$



Read operation (riscv_regfile.v)

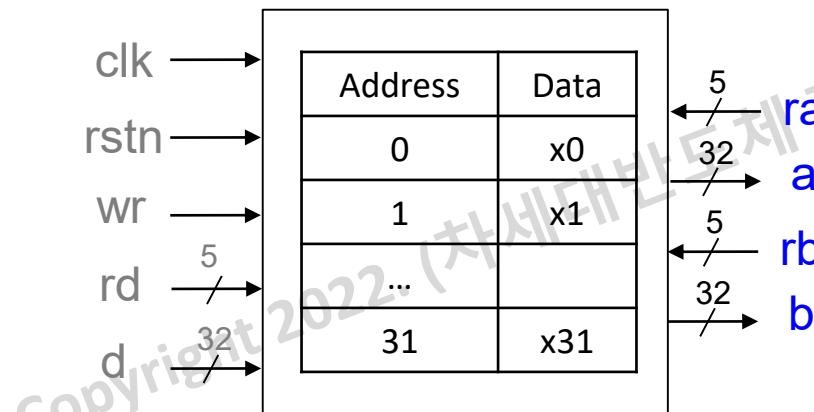- There are two read ports which use two address ra and rb.
- Use a "case" structure to check a given read address



```
reg [31:0] ra0_value_r;
reg [31:0] rb0_value_r;
always @ * begin
    case (ra0_i)
        5'd1: ra0_value_r = reg_r1_q;
        5'd2: ra0_value_r = reg_r2_q;
        ...
        5'd31: ra0_value_r = reg_r31_q;
        default : ra0_value_r = 32'h00000000;
    endcase

```

- asynchronous read by a given read address
- default value set to zero

```
case (rb0_i)
    5'd1: rb0_value_r = reg_r1_q;
    5'd2: rb0_value_r = reg_r2_q;
    ...
    5'd31: rb0_value_r = reg_r31_q;
    default : rb0_value_r = 32'h00000000;
endcase
end
```

read data outputs
based on an address

```
assign ra0_value_o = ra0_value_r;
assign rb0_value_o = rb0_value_r;
signal assignment
for output ports
endmodule //module description ends with "endmodule"
```

Test bench (riscv_regfile_tb.v)

- riscv_regfile_tb.v
 - Signals
 - Unit under test: riscv_regfile.v
 - Clock module
 - Reset module
 - Test cases

```
'timescale 1ns / 100ps
module riscv_regfile_tb;
    wire [31:0] ra0_value_o, rb0_value_o; //**** module output
    reg [4:0] ra0_i, rb0_i; //**** module inputs
    reg [4:0] rd0_i;
    reg [31:0] rd0_value_i;
    reg wr, clk, rstn;
```

```
riscv_regfile u_riscv_regfile
(
    .clk_i(clk),
    .rstn_i(rstn),
    .ra0_i(ra0_i),
    .rb0_i(rb0_i),
    .rd0_i(rd0_i),
    .rd0_value_i(rd0_value_i),
    .wr(wr),
    .ra0_value_o(ra0_value_o),
    .rb0_value_o(rb0_value_o)
);
```

Unit under test

```
initial forever
#5 clk = ~clk;
initial begin
    clk=1;
    rstn = 0;
    #20      rstn = 1;
```

Clock and reset
signals generation

Test bench (riscv_regfile_tb.v)

- Test case
 - Write operation
 - Set values for a write address rd
 - Set a write-enable signal (wr)
 - Read operation
 - Set values for the read addresses ra and rb
 - Monitor the outputs at ra_value, rb_value

```
ra0_i = 5'b00000;          // Select R0
rb0_i = 5'b00001;          // Select R1

#20    rd0_value_i = 32'h1234; // data to write
#20    wr = 1;                // write enable
      rd0_i = 5'b00001;        // addressing R1 to write
#10    wr = 0;                write operations

#20    rb0_i = 5'b00111;        // addressing R7 to read
      rd0_i = 5'b00111;        // new address to write
#20    rd0_value_i = 32'h5678; // new data to write
#20    wr = 1;                // write enable
#10    wr = 0;                // disabled
```

```
#20    ra0_i = 5'b00100;        // Read R4
      rb0_i = 5'b00101;        // Read R5
                                         read operations

#20    ra0_i = 5'b00111;        // Read R7
#20    rb0_i = 5'b00001;        // Read R1

#20
#20    rstn = 0;
#20    rstn = 1;
end
endmodule
                                         // testbench module ends
```

Waveform


- Write operation
 - Write to R1
 - $rd0_value \leftarrow \text{new value}$
 - $rd0 \leftarrow \text{new address (R1)}$

```
// WRITE
ra0_i = 5'b00000;           // Select R0
rb0_i = 5'b00001;           // Select R1

#20  rd0_value_i = 32'h1234;
#20  wr = 1;                  // write to R1
    rd0_i = 5'b00001;
#10  wr = 0;

#20  rb0_i = 5'b00111;         // Select R7
    rd0_i = 5'b00111;
#20  rd0_value_i = 32'h5678;
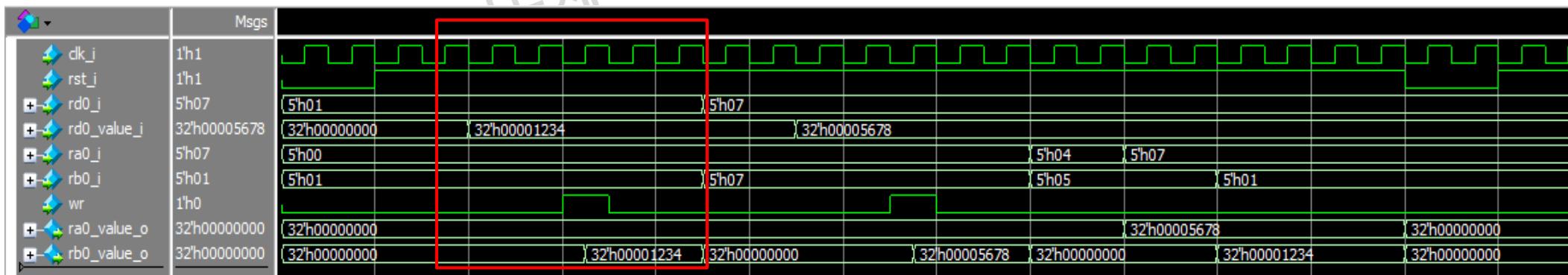
#20  wr = 1;                  // write to R7
#10  wr = 0;
```



Waveform


- Write operation
 - Write to R7
 - $rd0_value \leftarrow \text{new value}$
 - $rd0 \leftarrow \text{new address (R7)}$

```
// WRITE
ra0_i = 5'b0000;           // Select R0
rb0_i = 5'b0001;           // Select R1

#20    rd0_value_i = 32'h1234;
#20    wr = 1;                  // write to R1
      rd0_i = 5'b0001;
#10    wr = 0;

#20    rb0_i = 5'b0111;         // Select R7
      rd0_i = 5'b0111;
#20    rd0_value_i = 32'h5678;
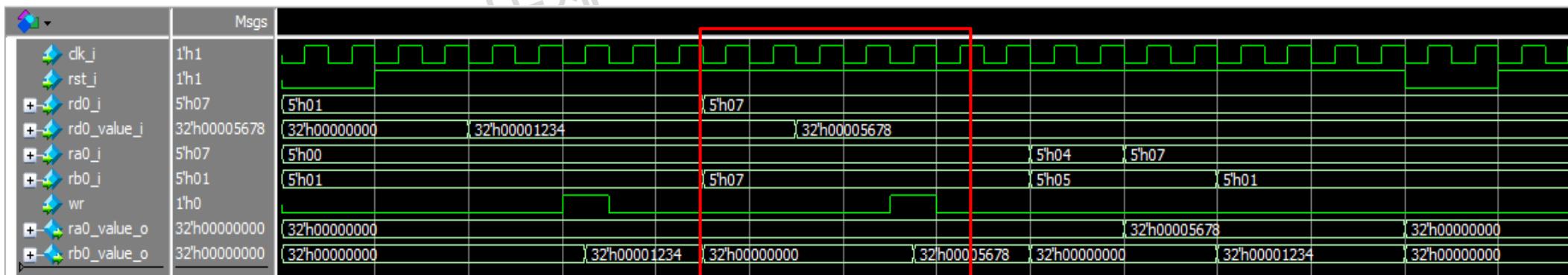
#20    wr = 1;                  // write to R7
#10    wr = 0;
```



Waveform


- Read operation
 - Read R4, R5
 - $ra_0_i \leftarrow$ new address (R4)
 - $rb_0_i \leftarrow$ new address (R5)

```
// READ
////////////////// READ //////////////////

#20    ra0_i = 5'b00100;          // Read R4
       rb0_i = 5'b00101;          // Read R5

#20    ra0_i = 5'b00111;          // Read R7
#20    rb0_i = 5'b00001;          // Read R1
///////////////////////////////
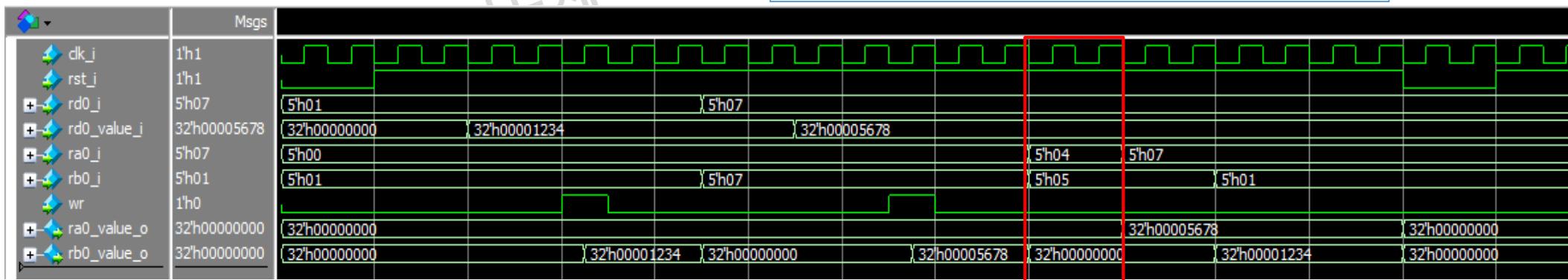
#20
#20    rstn = 0;
#20    rstn = 1;
```




Waveform

- Read operation
 - Read R7, R1
 - $ra_0_i \leftarrow$ new address (R7)
 - $rb_0_i \leftarrow$ new address (R1)

```
// READ
////////////////// READ //////////////////

#20    ra0_i = 5'b00100;          // Read R4
#20    rb0_i = 5'b00101;          // Read R5
#20    ra0_i = 5'b00111;          // Read R7
#20    rb0_i = 5'b00001;          // Read R1
////////////////// READ //////////////////
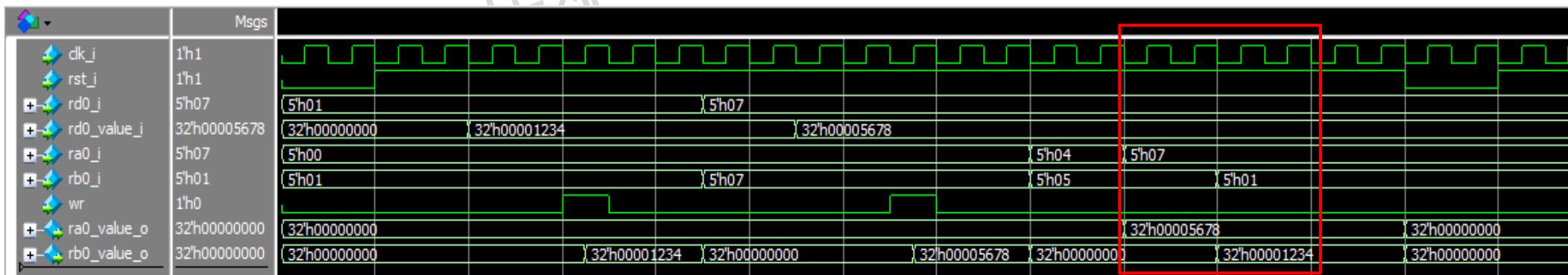
#20
#20    rstn = 0;
#20    rstn = 1;
```



Reset

- Often occurs when starting a system
 - ~ restart a PC
 - Registers are assigned to default values
- Reset
 - Reset register values
 - R7, R1


```
// READ
////////////////// READ //////////////////

#20 ra0_i = 5'b00100;           // Read R4
#20 rb0_i = 5'b00101;           // Read R5
#20 ra0_i = 5'b00111;           // Read R7
#20 rb0_i = 5'b00001;           // Read R1

///////////////////////////////



#20
#20 rstn = 0;
#20 rstn = 1;
```

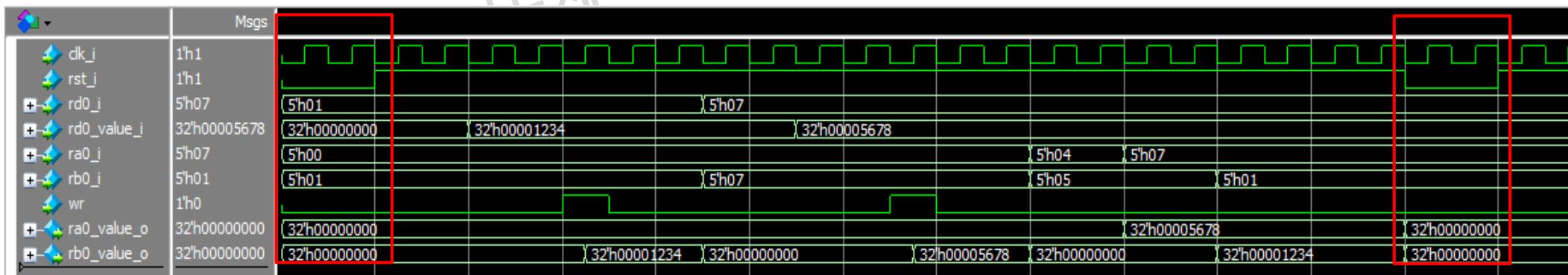

TODO: ...

- Implement riscv_regfile.v by completing the missing codes
 - Write operation
- Do a simulation with time = 300ns
- Show the output waveform

```
always @ (posedge clk_i or negedge rstn_i)
//-----
//**** reset value "0" for initialization
//    : all defined registers set to zero
//-----
if (!rstn_i) begin
    reg_r1_q      <= 32'h00000000;
    reg_r2_q      <= 32'h00000000;
    reg_r3_q      <= 32'h00000000;
    /*Insert your code */
    //reg_r4_q
    //reg_r5_q
    //reg_r6_q
    //reg_r7_q
    //*****
    reg_r8_q      <= 32'h00000000;
    reg_r9_q      <= 32'h00000000;
    reg_r10_q     <= 32'h00000000;
    reg_r11_q     <= 32'h00000000;
    reg_r12_q     <= 32'h00000000;
    reg_r13_q     <= 32'h00000000;
    reg_r14_q     <= 32'h00000000;
    reg_r15_q     <= 32'h00000000;
    reg_r16_q     <= 32'h00000000;
    reg_r17_q     <= 32'h00000000;
    reg_r18_q     <= 32'h00000000;
    reg_r19_q     <= 32'h00000000;
    reg_r20_q     <= 32'h00000000;
    reg_r21_q     <= 32'h00000000;
    reg_r22_q     <= 32'h00000000;
    reg_r23_q     <= 32'h00000000;
    reg_r24_q     <= 32'h00000000;
    reg_r25_q     <= 32'h00000000;
    reg_r26_q     <= 32'h00000000;
    reg_r27_q     <= 32'h00000000;
    reg_r28_q     <= 32'h00000000;
    reg_r29_q     <= 32'h00000000;
    reg_r30_q     <= 32'h00000000;
    reg_r31_q     <= 32'h00000000;
end
else begin
    if(wr) begin
        if (rd0_i == 5'd1) reg_r1_q <= rd0_value_i;
        if (rd0_i == 5'd2) reg_r2_q <= rd0_value_i;
        if (rd0_i == 5'd3) reg_r3_q <= rd0_value_i;
        if (rd0_i == 5'd4) reg_r4_q <= rd0_value_i;
        if (rd0_i == 5'd5) reg_r5_q <= rd0_value_i;
        if (rd0_i == 5'd6) reg_r6_q <= rd0_value_i;
        if (rd0_i == 5'd7) reg_r7_q <= rd0_value_i;
        if (rd0_i == 5'd8) reg_r8_q <= rd0_value_i;
        if (rd0_i == 5'd9) reg_r9_q <= rd0_value_i;
        if (rd0_i == 5'd10) reg_r10_q <= rd0_value_i;
        if (rd0_i == 5'd11) reg_r11_q <= rd0_value_i;
        if (rd0_i == 5'd12) reg_r12_q <= rd0_value_i;
        if (rd0_i == 5'd13) reg_r13_q <= rd0_value_i;
        if (rd0_i == 5'd14) reg_r14_q <= rd0_value_i;
        if (rd0_i == 5'd15) reg_r15_q <= rd0_value_i;
        /*Insert your code */
        //if      (rd0_i == 5'd16)
        //if      (rd0_i == 5'd17)
        //if      (rd0_i == 5'd18)
        //if      (rd0_i == 5'd19)
        //*****
        if (rd0_i == 5'd20) reg_r20_q <= rd0_value_i;
        if (rd0_i == 5'd21) reg_r21_q <= rd0_value_i;
        if (rd0_i == 5'd22) reg_r22_q <= rd0_value_i;
        if (rd0_i == 5'd23) reg_r23_q <= rd0_value_i;
        if (rd0_i == 5'd24) reg_r24_q <= rd0_value_i;
        if (rd0_i == 5'd25) reg_r25_q <= rd0_value_i;
        if (rd0_i == 5'd26) reg_r26_q <= rd0_value_i;
        if (rd0_i == 5'd27) reg_r27_q <= rd0_value_i;
        if (rd0_i == 5'd28) reg_r28_q <= rd0_value_i;
        if (rd0_i == 5'd29) reg_r29_q <= rd0_value_i;
        if (rd0_i == 5'd30) reg_r30_q <= rd0_value_i;
        if (rd0_i == 5'd31) reg_r31_q <= rd0_value_i;
    end
end
```

Copyright 2022. (차세대반도체 혁신)

TODO: ...

- Implement riscv_regfile.v by completing the missing codes
 - Read operation
- Do a simulation with time = 300ns
- Show the output waveform

```
reg [31:0] ra0_value_r;
reg [31:0] rb0_value_r;
always @ *
begin
    case (ra0_i)
        //*****
        // 5'd1: ra0_value_r = reg_r1_q; //*****
        // 5'd2: ra0_value_r = reg_r2_q;
        // 5'd3: ra0_value_r = reg_r3_q;
        // 5'd4: ra0_value_r = reg_r4_q;
        // 5'd5: ra0_value_r = reg_r5_q;
        // 5'd6: ra0_value_r = reg_r6_q;
        // 5'd7: ra0_value_r = reg_r7_q;
        // 5'd8: ra0_value_r = reg_r8_q;
        // 5'd9: ra0_value_r = reg_r9_q;
        /*Insert your code */
        //5'd10:
        //5'd11:
        //5'd12:
        //5'd13:
        //***** */
        5'd14: ra0_value_r = reg_r14_q;
        5'd15: ra0_value_r = reg_r15_q;
        5'd16: ra0_value_r = reg_r16_q;
        5'd17: ra0_value_r = reg_r17_q;
        5'd18: ra0_value_r = reg_r18_q;
        5'd19: ra0_value_r = reg_r19_q;
        5'd20: ra0_value_r = reg_r20_q;
        5'd21: ra0_value_r = reg_r21_q;
        5'd22: ra0_value_r = reg_r22_q;
        5'd23: ra0_value_r = reg_r23_q;
        5'd24: ra0_value_r = reg_r24_q;
        5'd25: ra0_value_r = reg_r25_q;
        5'd26: ra0_value_r = reg_r26_q;
        5'd27: ra0_value_r = reg_r27_q;
        5'd28: ra0_value_r = reg_r28_q;
        5'd29: ra0_value_r = reg_r29_q;
        5'd30: ra0_value_r = reg_r30_q;
        5'd31: ra0_value_r = reg_r31_q;
        default : ra0_value_r = 32'h00000000;
    endcase

```

```
case (rb0_i)
5'd1: rb0_value_r = reg_r1_q;
5'd2: rb0_value_r = reg_r2_q;
5'd3: rb0_value_r = reg_r3_q;
5'd4: rb0_value_r = reg_r4_q;
5'd5: rb0_value_r = reg_r5_q;
5'd6: rb0_value_r = reg_r6_q;
/*Insert your code */
//5'd7:
//5'd8:
//5'd9:
//5'd10:
//***** */
5'd11: rb0_value_r = reg_r11_q;
5'd12: rb0_value_r = reg_r12_q;
5'd13: rb0_value_r = reg_r13_q;
5'd14: rb0_value_r = reg_r14_q;
5'd15: rb0_value_r = reg_r15_q;
5'd16: rb0_value_r = reg_r16_q;
5'd17: rb0_value_r = reg_r17_q;
5'd18: rb0_value_r = reg_r18_q;
5'd19: rb0_value_r = reg_r19_q;
5'd20: rb0_value_r = reg_r20_q;
5'd21: rb0_value_r = reg_r21_q;
5'd22: rb0_value_r = reg_r22_q;
5'd23: rb0_value_r = reg_r23_q;
5'd24: rb0_value_r = reg_r24_q;
5'd25: rb0_value_r = reg_r25_q;
5'd26: rb0_value_r = reg_r26_q;
5'd27: rb0_value_r = reg_r27_q;
5'd28: rb0_value_r = reg_r28_q;
5'd29: rb0_value_r = reg_r29_q;
5'd30: rb0_value_r = reg_r30_q;
5'd31: rb0_value_r = reg_r31_q;
default : rb0_value_r = 32'h00000000;
endcase
```


Lab 2: Arithmetic Logic Unit (ALU)

- Lab 2: Design an ALU
 - Implement an ALU module
 - Run simulation
 - Show the output result

Copyright 2022. (차세대반도체 혁신공유대학 사업단) all rights reserved.

ALU structure

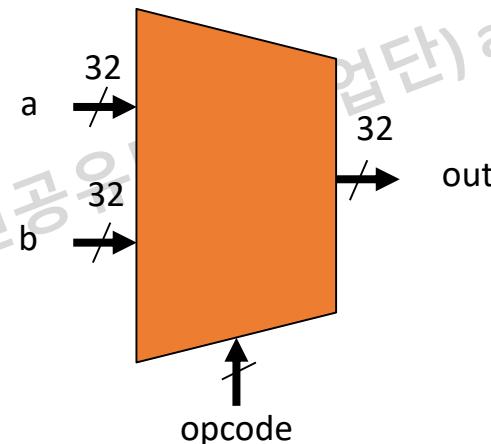
- Inputs: two 32-bit operands and one 4-bit operation code (opcode)
- Output: 32-bit result
- Pseudocode
 - Case (opcode)
 - ADD
 - SUB
 - AND
 - OR
 - SLL
 - SRL
 -
 - Endcase



Port declaration (riscv_alu.v)

- Inputs: two 32-bit operands and one 4-bit operation code (opcode)
- Output: 32-bit result
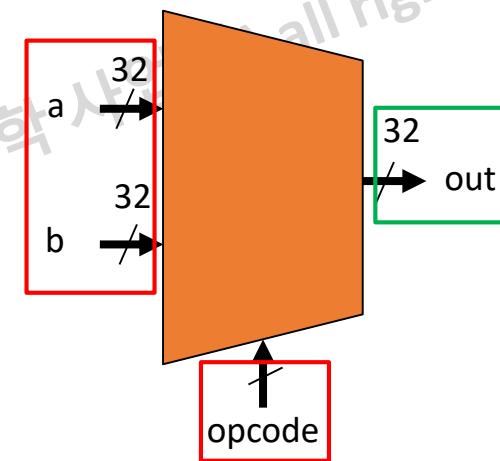
```
module riscv_alu
(
    // Inputs
    input [ 3:0] alu_op_i,
    input [31:0] alu_a_i,
    input [31:0] alu_b_i,
    // Outputs
    output [31:0] alu_p_o
);
```



Logics (riscv_alu.v)

- Pseudocode
 - Case (opcode)
 - ADD
 - SUB
 - AND
 - OR
 - SLL
 - SRL
 -
 - Endcase

```
always @ (alu_op_i or alu_a_i or alu_b_i or sub_res_w)
begin
    shift_right_fill_r = 16'b0;
    shift_right_1_r = 32'b0;
    ...
    shift_left_1_r = 32'b0;
    ...
    case (alu_op_i)
        `ALU_SHL:           // Shift Left  shift left operation by 32bit operand b cases (shift left 1 to 31)
        begin
            if (alu_b_i[0] == 1'b1)
                shift_left_1_r = {alu_a_i[30:0],1'b0};
            else
                shift_left_1_r = alu_a_i;
            ...
        end
    end
```

Shift operation


- Shift operations
 - Left: $\text{out} = \text{a} \ll \text{b}$
 - Right: $\text{out} = \text{a} \gg \text{b}$
- Both a and b are 32-bit registers
- Question: What is the number of possible outcomes?
 - 0, 1, 2, ..., $2^{32}-1$

Shift operation

- Shift operations
 - Left: $\text{out} = \text{a} \ll \text{b}$
 - Right: $\text{out} = \text{a} \gg \text{b}$
- Both a and b are 32-bit registers
- Question: What is the number of possible outcomes?
 - 0, 1, 2, ..., $2^{32} - 1$ because a is a 32-bit number


Shift operation: Naïve implementation

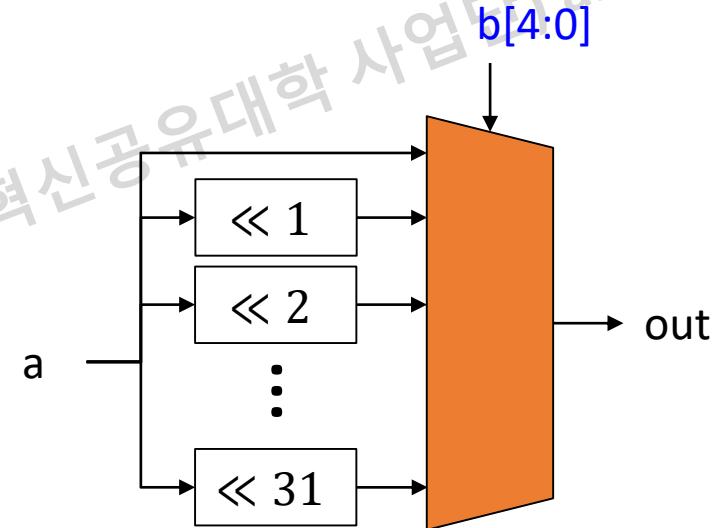- Shift operations
 - Left: $\text{out} = \text{a} \ll \text{b}$
 - Right: $\text{out} = \text{a} \gg \text{b}$
- Both a and b are 32-bit registers
- Question: What is the number of possible outcomes?
 - 0, 1, 2, ..., $2^{32}-1$ because a is a **32-bit** number
 $\Rightarrow \text{b}[31:5] \neq 0 \rightarrow \text{out} = 0$
- Pseudocode
 - Case ($\text{b}[4:0]$)
 - 0
 - 1
 - ...
 - 31
 - End case



Shift operation: Barrel implementation

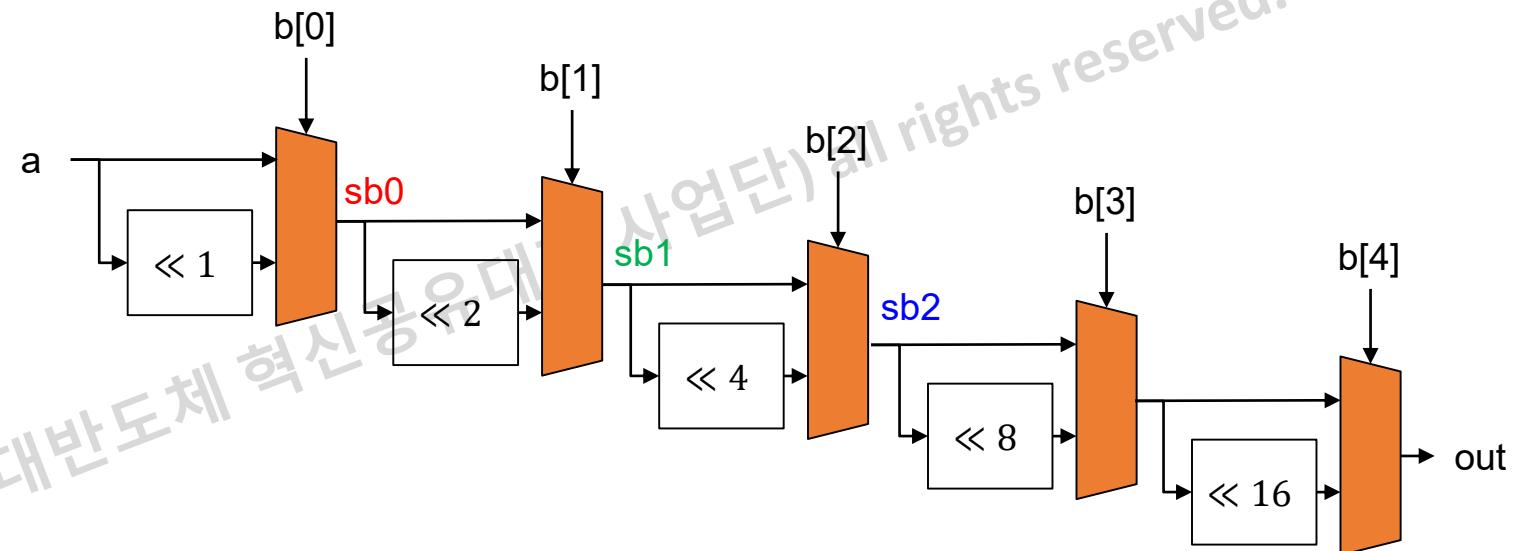- $b \in \{0, 1, 2, \dots, 31\} \Rightarrow b[4:0]$
- Pseudocode for Barrel shift implementation
 - If $b[0] == 1$
 $sb0 \leftarrow (a \ll 1)$
 - Else
 $sb0 \leftarrow a$
 - If $b[1] == 1$
 $sb1 \leftarrow (sb0 \ll 2)$
 - Else
 $sb1 \leftarrow sb0$
 - If $b[2] == 1$
 $sb2 \leftarrow (sb1 \ll 4)$
 - Else
 $sb2 \leftarrow sb1$
 - ...



TODO: ...

- Implement riscv_alu.v codes by completing some missing codes
- Do a simulation with time = 400ns
- Show the waveform

```
-----
// Shift Right Logical and Shift Right arithmetic
-----
`ALU_SRL,`ALU_SRA :
begin
    // Arithmetic shift? Fill with 1's if MSB set
    if (alu_a_i[31] == 1'b1 && alu_op_i == `ALU_SRA)
        shift_right_fill_r = 16'b1111111111111111;
    else
        shift_right_fill_r = 16'b0000000000000000;

    // Insert your code here
    //{{{
    //if (alu_b_i[0] == 1'b1)
    //    shift_right_1_r = /*Insert your code */
    //else
    //    shift_right_1_r = /*Insert your code */

    //if (alu_b_i[1] == 1'b1)
    //    shift_right_2_r = /*Insert your code */
    //else
    //    shift_right_2_r = /*Insert your code */
    //}}}
```

```
case (alu_op_i)
-----
// Shift Left Logical
-----
`ALU_SLL :
begin
    if (alu_b_i[0] == 1'b1)
        shift_left_1_r = {alu_a_i[30:0],1'b0};
    else
        shift_left_1_r = alu_a_i;

    if (alu_b_i[1] == 1'b1)
        shift_left_2_r = {shift_left_1_r[29:0],2'b00};
    else
        shift_left_2_r = shift_left_1_r;

    // Insert your code here
    //{{{
    //if (alu_b_i[2] == 1'b1)
    //    shift_left_4_r = /*Insert your code */
    //else
    //    shift_left_4_r = /*Insert your code */

    //if (alu_b_i[3] == 1'b1)
    //    shift_left_8_r = /*Insert your code */
    //else
    //    shift_left_8_r = /*Insert your code */
    //}}}

    if (alu_b_i[4] == 1'b1)
        result_r = {shift_left_8_r[15:0],16'b0000000000000000};
    else
        result_r = shift_left_8_r;
```

TODO: ...

- Implement riscv_alu.v codes by completing some missing codes
- Do a simulation with time = 400ns
- Show the waveform

```
//-----
// Logical
//-----
`ALU_AND :
begin
    result_r      = (alu_a_i & alu_b_i);
end
`ALU_OR  :
begin
    //result_r      = /*Insert your code */
end
`ALU_XOR :
begin
    //result_r      = /*Insert your code */
end
//-----
// Comparision
//-----
`ALU_SLTU : // Unsigned number
begin
    result_r      = (alu_a_i < alu_b_i) ? 32'hl : 32'h0;
end
`ALU_SLT : // Signed numbers
begin
    //Insert your code
    //{{{
    //if (alu_a_i[31] != alu_b_i[31])
    //    result_r  = /*Insert your code */
    //else
    //    result_r  = sub_res_w[31] ? 32'hl : 32'h0;
    //}}}
end
```

Operation definition (riscv_defines.v)

- Operation definition
 - Shift, shift arithmetic
 - Arithmetic operations: ADD, SUB.
 - Logic operations: AND, OR, XOR
 - Compare operations: Less than, less than with signed.

```
`define ALU_ADD 4'd0      // Addition
`define ALU_SUB 4'd1      // Subtraction
`define ALU_AND 4'd2      // AND
`define ALU_OR 4'd3       // OR
`define ALU_XOR 4'd4      // XOR
`define ALU_SLT 4'd5      // Compare, Signed
`define ALU_SLTU 4'd6     // Compare, Unsigned
`define ALU_SLL 4'd7      // Shift Left Logical
`define ALU_SRL 4'd8      // Shift Right Logical
`define ALU_SRA 4'd9      // Shift Right Arithmetic
`define ALU_MULL 4'd10    // Multiplier Upper Half
`define ALU_MULH 4'd11    // Multiplier Upper Half
`define ALU_DIV 4'd12     // Divider, division
`define ALU_Rem 4'd13     // Divider, quotient
`define ALU_AUIPC 4'd14   // Add Upper Imm to PC
`define ALU_IDLE 4'd15
```

Test bench (riscv_alu_tb.v)

```
module riscv_alu_tb();  
    reg rstn;  
    reg clk;  
    reg [3:0] alu_op_i;  
    reg [31:0] alu_a_i  
    reg [31:0] alu_b_i;  
    wire [31:0] alu_p_o;
```

```
riscv_alu u_alu (  
    .alu_op_i(alu_op_i),  
    .alu_a_i(alu_a_i),  
    .alu_b_i(alu_b_i),  
    .alu_p_o(alu_p_o)  
);
```

module instance for test bench

```
parameter p=10;  
initial  
begin  
    clk = 1'b0;  
    forever #p clk = !clk;  
end  
  
initial begin  
    rstn = 1'b0;          // negedge reset on  
    #(4*p) rst = 1'b1;    // negedge reset off  
end
```

Test cases

```
initial begin
    #(8*p)    alu_a_i = 32'h0;
    alu_b_i = 32'h0;
    alu_op_i = `ALU_LESS_THAN;

    #(4*p)    alu_a_i = 32'd2020;
    alu_b_i = 32'd2021;
    alu_op_i = `ALU_ADD;
    #(2*p)    alu_op_i = `ALU_SUB;

    #(2*p)    alu_op_i = `ALU_AND;
    #(2*p)    alu_op_i = `ALU_OR;
    #(2*p)    alu_op_i = `ALU_XOR;

end

endmodule
```


Copyright 202

Waveform

- Insert operands (from Register File)
- Insert operations
 - Comparison

```
#(8*p)
    alu_a_i = 32'h0;
    alu_b_i = 32'h0;
    alu_op_i = `ALU_LESS_THAN;

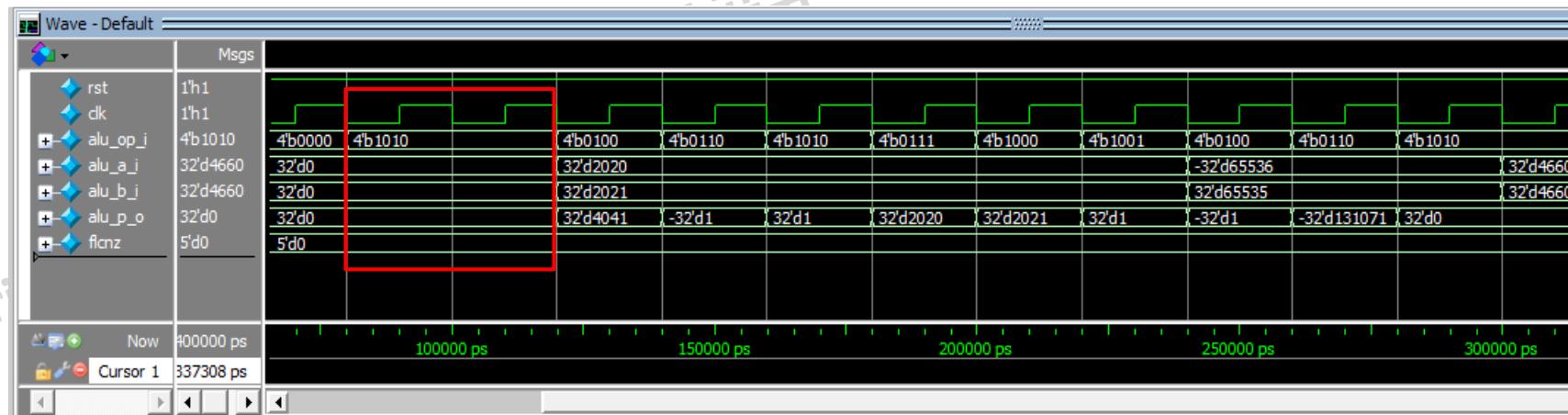
#(4*p)
    alu_a_i = 32'd2020;
    alu_b_i = 32'd2021;
    alu_op_i = `ALU_ADD;
#(2*p) alu_op_i = `ALU_SUB;
#(2*p) alu_op_i = `ALU_AND;
#(2*p) alu_op_i = `ALU_OR;
#(2*p) alu_op_i = `ALU_XOR;
```



Waveform

- Insert operands (from Register File)
- Insert operations
 - Add
 - Subtraction

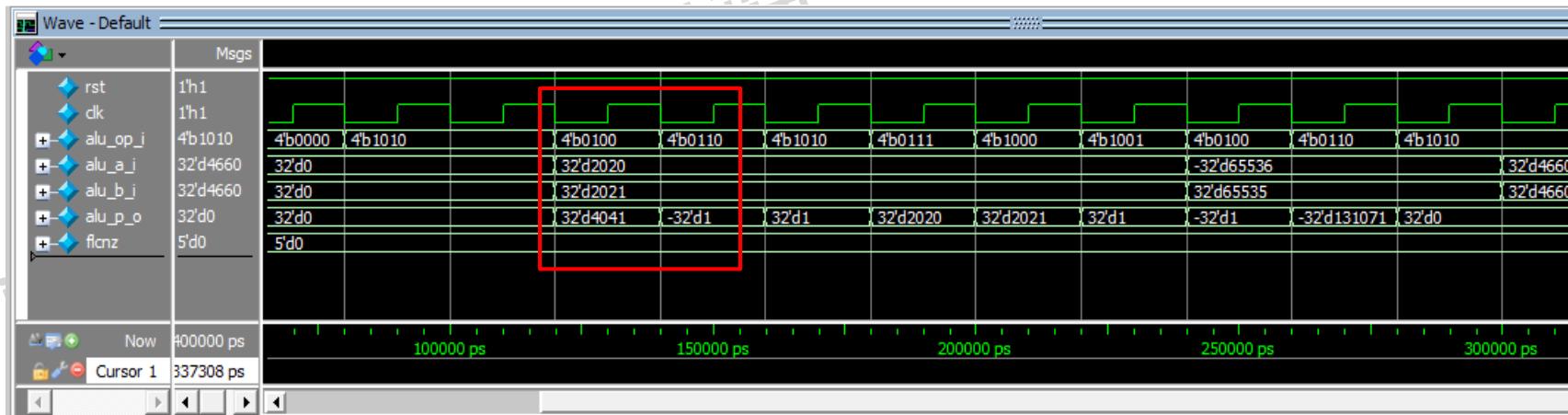
```
#(8*p)
    alu_a_i = 32'h0;
    alu_b_i = 32'h0;
    alu_op_i = `ALU_LESS_THAN;
#(4*p)
    alu_a_i = 32'd2020;
    alu_b_i = 32'd2021;
    alu_op_i = `ALU_ADD;
#(2*p) alu_op_i = `ALU_SUB;
#(2*p) alu_op_i = `ALU_AND;
#(2*p) alu_op_i = `ALU_OR;
#(2*p) alu_op_i = `ALU_XOR;
```



Waveform

- Insert operands (from Register File)
- Insert operations
 - AND
 - OR
 - XOR
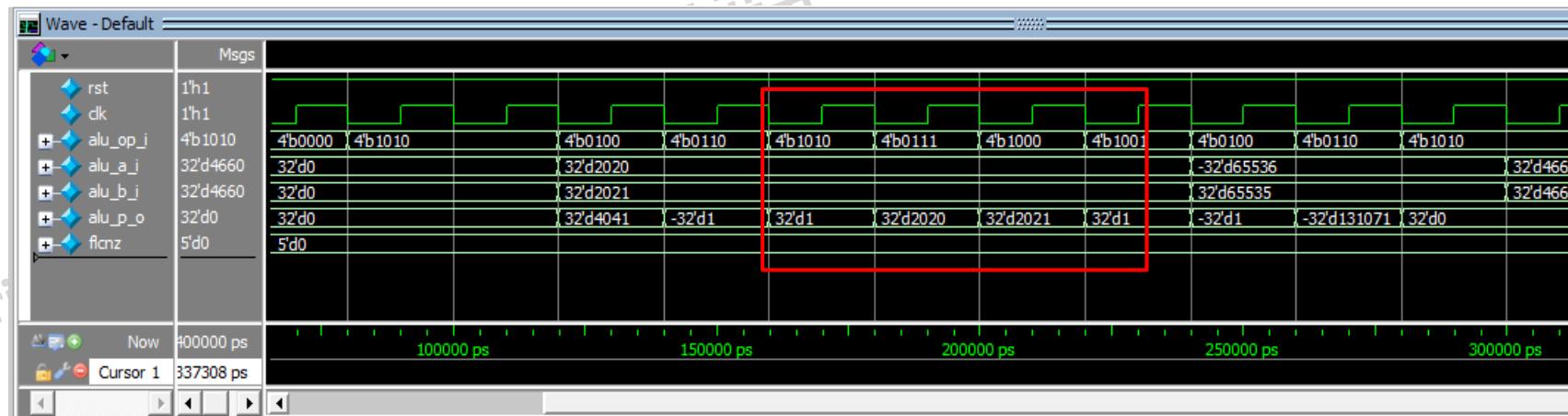
```
#(8*p)
    alu_a_i = 32'h0;
    alu_b_i = 32'h0;
    alu_op_i = `ALU_LESS_THAN;
#(4*p)
    alu_a_i = 32'd2020;
    alu_b_i = 32'd2021;
    alu_op_i = `ALU_ADD;
#(2*p) alu_op_i = `ALU_SUB;
#(2*p) alu_op_i = `ALU_AND;
#(2*p) alu_op_i = `ALU_OR;
#(2*p) alu_op_i = `ALU_XOR;
```



Test bench

- Display the results of test cases.
 - `$display`: a function to print out a message
 - `$realtime`: a function to show a time stamp

```
-----  
// ALU operations  
-----  
#(8*p)  
    alu_a_i = 32'h0000_2222;  
    alu_b_i = 32'h0000_2222;  
    alu_op_i = `ALU_SLTU;  
#(p) $display("T=%03t ns: %h < %h : %h (Unsigned)\n", $realtime/1000, alu_a_i, alu_b_i, alu_p_o);  
  
// Addition  
#(4*p)  
    alu_a_i = 32'h0000_1111;  
    alu_b_i = 32'h0000_1111;  
    alu_op_i = `ALU_ADD;  
#(p) $display("T=%03t ns: %h + %h = %h\n", $realtime/1000, alu_a_i, alu_b_i, alu_p_o);  
  
// Subtraction  
#(2*p) alu_op_i = `ALU_SUB;  
#(p) $display("T=%03t ns: %h - %h = %h\n", $realtime/1000, alu_a_i, alu_b_i, alu_p_o);  
  
// Comparison  
#(2*p) alu_op_i = `ALU_SLTU;  
#(p) $display("T=%03t ns: %h < %h = %h\n", $realtime/1000, alu_a_i, alu_b_i, alu_p_o);
```

Test bench

- Display the results of test cases.
 - \$display: a function to print out a message
 - \$realtime: a function to show a time stamp

```
//-----  
// ALU operations  
//-----  
  
#(8*p)  
  alu_a_i = 32'h0000  
  alu_b_i = 32'h0000  
  alu_op_i = `ALU_SI  
#(p)  $display("T=%03t r  
  
// Addition  
#(4*p)  
  alu_a_i = 32'h0000  
  alu_b_i = 32'h0000  
  alu_op_i = `ALU_ADD  
#(p)  $display("T=%03t r  
  
// Subtraction  
#(2*p) alu_op_i = `ALU_SUB  
#(p)  $display("T=%03t r  
  
// Comparison  
#(2*p) alu_op_i = `ALU_SIT  
#(p)  $display("T=%03t r  
VSIM 33> run 1000ns  
# T=290 ns: 00002222 < 00002222 : 00000000 (Unsigned)  
#  
# T=340 ns: 00001111 + 00001111 = 00002222  
#  
# T=370 ns: 00001111 - 00001111 = 00000000  
#  
# T=400 ns: 00001111 < 00001111 = 00000000  
#  
# T=450 ns: 00001110 & 00000111 = 00000110  
#  
# T=480 ns: 00001110 | 00000111 = 00001111  
#  
# T=510 ns: 00001110 ^ 00000111 = 00001001  
#
```

+ ,
 ()
 01
 a < b



Lab 3: Multiplier

- Lab 3: Design a sequential multiplier
 - Implement a sequential multiplier module
 - Create a test bench
 - Run simulation
 - Show the output result

Copyright 2022. (차세대반도체 혁신공유대학 사업단) all rights reserved.

Multiplier

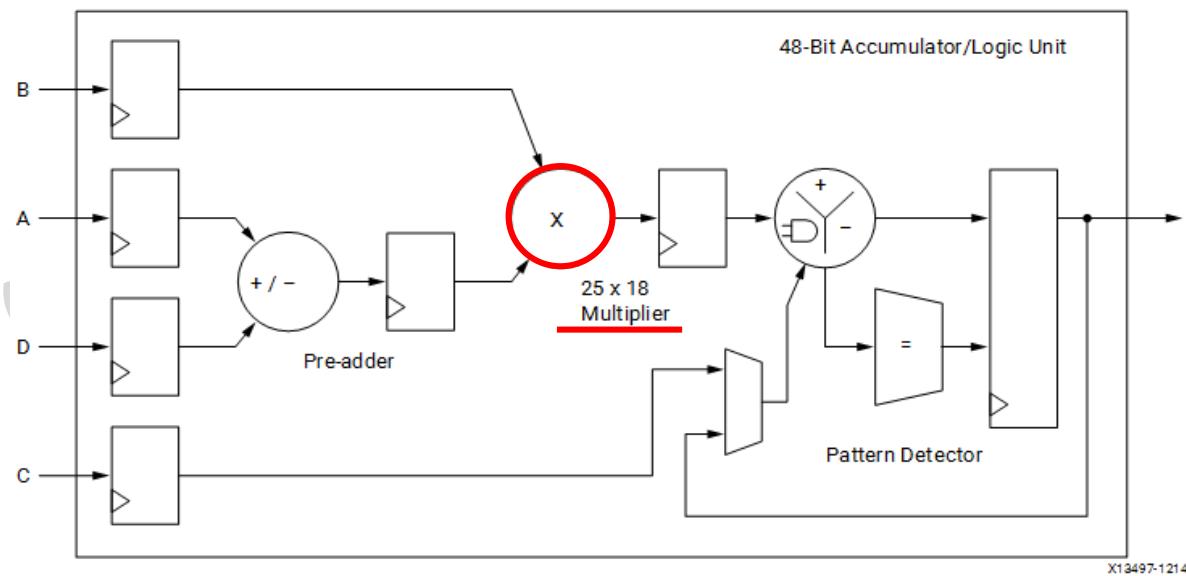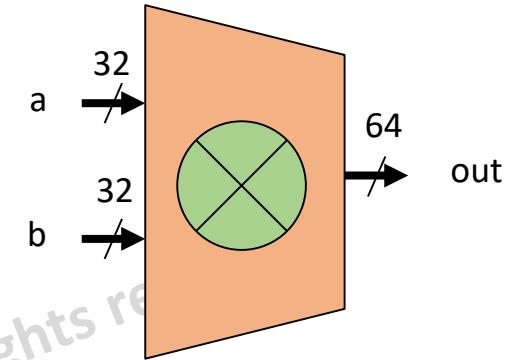- Multiplier out = $a \times b$
 - a and b are 32-bit integers; out is a 64-bit integer.
- How to implement a multiplier in H/W?
 - Simply use a "*" operation
 - Dedicated multiplier circuit (DSP)
 - Design a customized multiplier



Multiplier (riscv_multiplier.v)

```
module riscv_multiplier
(
    // Inputs
    input clk_i,
    input rstn_i,
    input [3:0] id_alu_op_r,
    input id_a_signed_r,
    input id_b_signed_r,
    input [31:0] id_ra_value_r, // 32bits multiplicand register a
    input [31:0] id_rb_value_r, // 32bits multiplier register b

    // Outputs
    output [63:0] mul_res_w,           // 64bits multiplier out
    output ex_stall_mul_w
);
```

```
reg      mul_busy_r;
reg      mul_ready_r;
reg [4:0] mul_count_r;
reg [63:0] mul_res_r;
wire     mul_request_w;
wire [32:0] mul_sum_w;
```

Multiplier

- Multiplier out = $a \times b$
 - a, b are 32-bit integers; out is a 64-bit integer.
- Decompose a multiplier into multiple sequential adders and shifters
 - $t = 1$: out = $b[0] \times a$
 - $t = 2$: out = $((b[1] \times a) \ll 1) + \text{out}$
 -
 - $t = 32$: out = $((b[31] \times a) \ll 31) + \text{out}$

Sequential multiplier

- Pseudocode

```
mul_sum_w = { 1'b0, mul_res_r[63:32] } + { 1'b0, mul_res_r[0] ? b : 32'h0 }
if mul_busy
    count ← count – 1
    mul_res_r ← { mul_sum_w, mul_res_r[31:1] };
    if count == 0
        mul_busy ← 0
    end
end
else if (mul_ready_r)
    mul_ready_r <= 1'b0;
end
else if mul_req
    count ← 31
    mul_busy ← 1
    mul_res_r ← { 32'h0, a};
end
```

Sequential multiplier

- Pseudocode

```
mul_sum_w = { 1'b0, mul_res_r[63:32] } + { 1'b0, mul_res_r[0] ? b : 32'h0 }
if mul_busy
    count ← count – 1
    mul_res_r ← { mul_sum_w, mul_res_r[31:1] };
    if count == 0
        mul_busy ← 0
    end
end
else if (mul_ready_r)
    mul_ready_r <= 1'b0;
end
else if mul_req
    count ← 31
    mul_busy ← 1
    mul_res_r ← { 32'h0, a};
end
```

- Start a multiplication request
 - Initialize a counter
 - Indicate that it is busy
 - Initialize the accumulate result

Sequential multiplier

- Pseudocode

```
mul_sum_w = { 1'b0, mul_res_r[63:32] } + { 1'b0, mul_res_r[0] ? b : 32'h0 }
if mul_busy
    count ← count – 1
    mul_res_r ← { mul_sum_w, mul_res_r[31:1] };
    if count == 0
        mul_busy ← 0
    end
end
else if (mul_ready_r)
    mul_ready_r <= 1'b0;
end
else if mul_req
    count ← 31
    mul_busy ← 1
    mul_res_r ← { 32'h0, a};
end
```

- Do multiplication
- Update a counter
- Update a busy flag

Explanation

```
assign mul_sum_w = { 1'b0, mul_res_r[63:32] } + { 1'b0, mul_res_r[0] ? mul_b_w : 32'h0 };
assign mul_res_w = mul_negative_w ? -mul_res_r : mul_res_r;

always @(posedge clk_i, neg) begin
    if (~reset_i) begin
        mul_busy_r <= 1'b0;
        ...
    end
    else begin
        if (mul_busy_r) begin
            mul_count_r <= mul_count_r - 5'd1;
            ...
        end
        else if (mul_ready_r) begin
            mul_ready_r <= 1'b0;
        end
        else if (mul_request_w) begin
            mul_count_r <= 5'd31;
            ...
        end
    end
end

assign mul_request_w = (`ALU_MULL == id_alu_op_r || `ALU_MULH == id_alu_op_r);
assign ex_stall_mul_w = mul_request_w && !mul_ready_r;

endmodule
```

TODO: ...

- Implement riscv_multiplier.v by completing some missing codes
- Do a simulation with time = 1000ns
- Show the waveform

```
always @(posedge clk_i or negedge rstn_i) begin
    if (~rstn_i) begin
        mul_busy_r <= 1'b0;
        mul_ready_r <= 1'b0;
        mul_count_r <= 5'd0;
        mul_res_r <= 64'h0;
    end else begin
        if (mul_busy_r) begin
            //Insert your code
            //mul_count_r <= /*Insert your code */
            mul_res_r <= { mul_sum_w, mul_res_r[31:1] };

        if (mul_count_r == 5'd0) begin
            mul_busy_r <= 1'b0;
            // Insert your code
            // mul_ready_r <= /*Insert your code */
        end

        end else if (mul_ready_r) begin                //***
            mul_ready_r <= 1'b0;

        end else if (mul_request_w) begin             //***
            mul_count_r <= 5'd31;                      //***
            mul_busy_r <= 1'b1;                         //***
            // Insert your code
            //mul_res_r <= /*Insert your code */      //***
        end
    end
end
```

Test bench (riscv_multiplier_tb.v)

```
module multiplier_tb;
    reg rstn;
    reg clk;
    reg [3:0] alu_op_i;
    reg [31:0] alu_a_i, alu_b_i;
    wire [63:0] alu_p_o;
    wire ex_stall_mul_w;
    reg a_signed, b_signed;
```

```
parameter p=10;
initial begin
    clk = 1'b0;
    forever #(p/2) clk = !clk;
end
```

Fast

```
riscv_multiplier_fast
u_riscv_multiplier_fast(
    /*input */clk_i(clk),
    /*input */rstn_i(rstn),
    /*input [3:0] */id_alu_op_r(alu_op_i),
    /*input */id_a_signed_r(a_signed),
    /*input */id_b_signed_r(b_signed),
    /*input [31:0] */id_ra_value_r(alu_a_i),
    /*input [31:0] */id_rb_value_r(alu_b_i),
    /*output [63:0] */mul_res_w(alu_p_o_f),
    /*output */ex_stall_mul_w(ex_stall_mul_w_f)
);
```

Slow

```
// Sequential multiplier: 32 cycle delay
riscv_multiplier
u_riscv_multiplier(
    /*input */clk_i(clk),
    /*input */rstn_i(rstn),
    /*input [3:0] */id_alu_op_r(alu_op_i),
    /*input */id_a_signed_r(a_signed),
    /*input */id_b_signed_r(b_signed),
    /*input [31:0] */id_ra_value_r(alu_a_i),
    /*input [31:0] */id_rb_value_r(alu_b_i),
    /*output [63:0] */mul_res_w(alu_p_o),
    /*output */ex_stall_mul_w(ex_stall_mul_w)
);
```

Test cases (riscv_multiplier_tb.v)

```
initial begin
    rstn = 1'b0;                                // negedge reset on
    alu_a_i = 0;
    alu_b_i = 0;
    alu_op_i = 0;
    a_signed = 0;
    b_signed = 0;
    alu_op_i = `ALU_ADD;
    #(4*p) rstn = 1'b1;                         // negedge reset off
    #(2*p)      a_signed = 0;
                b_signed = 0;
                alu_a_i = 32'h00000008;
                alu_b_i = 32'h00000008;
    #(2*p)      alu_op_i = `ALU_MULL;

    #(p)        alu_op_i = `ALU_ADD;

    #(32*p)     alu_a_i = 32'h00000007;
                alu_b_i = 32'h00000009;
    #(2*p)      alu_op_i = `ALU_MULL;

    #(p)        alu_op_i = `ALU_ADD;
end
endmodule
```

- Test case 1: do 8×8


- Test case 2: do 7×9

ed.

Copyright

Waveform (Slow multiplier)

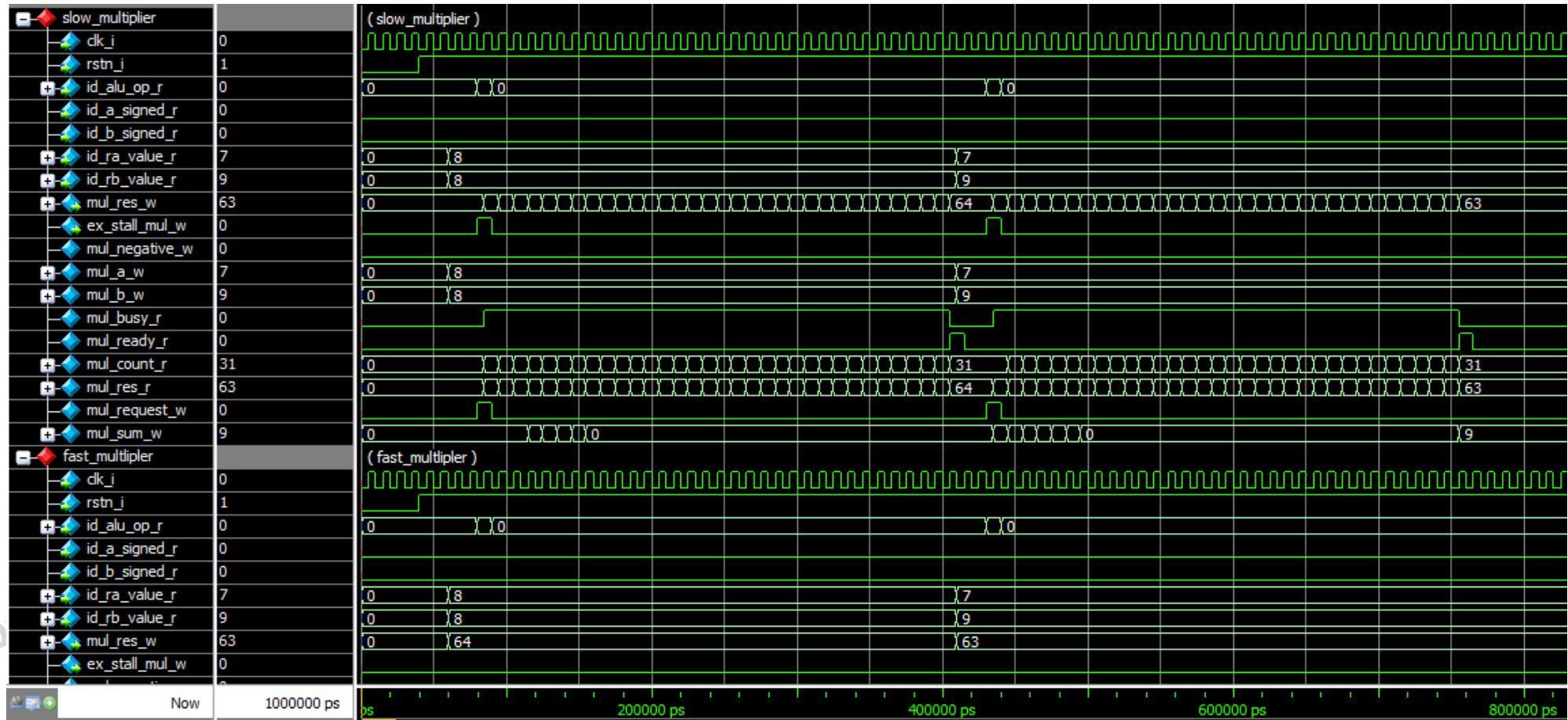- It takes 32 cycles to complete a multiplier



Questions

1. (Shifter) Compare two shifter implementations.
2. (Multiplier) How many cycles does a sequential (slow) multiplier take to complete a multiplication?

Why?

- 32 cycles
- Does the multiplier work correctly if *a new multiplication is issued during computation?*
- Does the multiplier work correctly if *the inputs are updated during computation?*